



HAM Radio Board of Education
NEVER STOP LEARNING

Antenna Summit

Sponsored by



Session 3 – Components

Chapter 4.1 to 4.5.6

+ Other Material



Instructor:

Phil Brunner – AE7OH (was K9DTD, W6GOL)

- ARRL HANDBOOK for Radio Communications
 - (Reference for detailed information)
- Q & A via Chat or at the end of each hour
- Email questions to: phil.brunner@gmail.com
- Viewgraphs are at HamRadioEdu.com

Chapter 4 – Components

- The World of electronics is changing rapidly
 - Landlines replaced by Cell Phone, Zoom, Skype
 - Vacuum Tubes Disappearing – (Light Bulbs, CRTs, Radio Tubes)
- Computers and DSPs are replacing individual components and units (e.g., Modems)
- We will concentrate on characteristics and skip the details!


Components Characteristics

- Practical Resistors, Capacitors and Inductors
- Transformers
- Semiconductors
- Circuit Simulation and Analysis Tools
- Examples

Resistors

- Wire size suitable for max current
- Resistance usually increases with temperature
- Component Resistors
 - Carbon, Metal-oxide
 - Wirewound- low-frequency due to inductance
 - Metal-film, Carbon-film – deposit on insulating substrate
- Power rating and temperature stability are considerations
- Tolerance often unimportant – 20%, 10%, 5%, 1%
- Potentiometers – variable resistors



Resistors

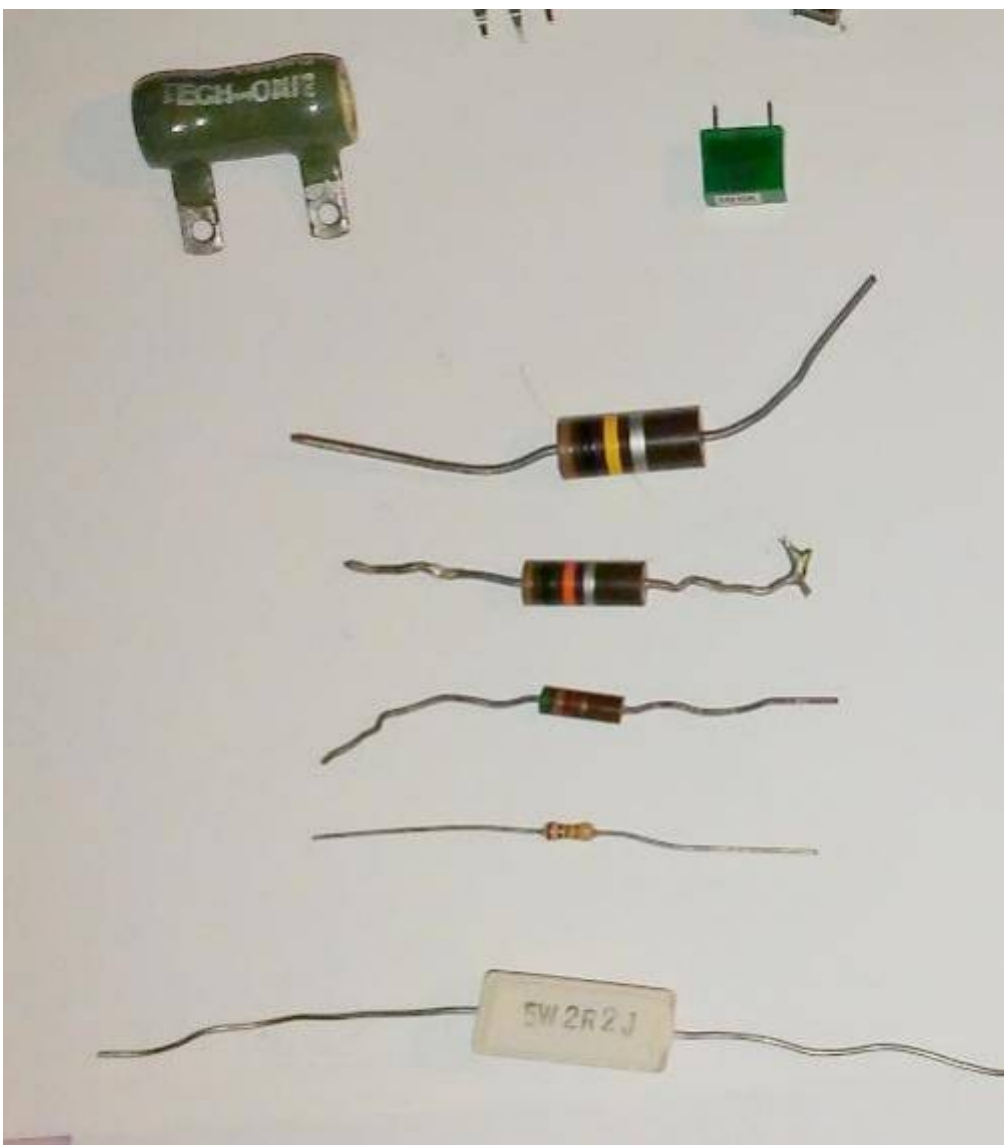

Capacitors

- Ideally blocks DC, no leakage, no energy loss
- Tolerance and temperature coefficient
- Voltage rating and breakdown
- Frequency, resistance, leakage, inductance considerations
- Ceramic, plastic film, mica, electrolytic, air-variable, vacuum
- Electrolytics are high capacity and polarized - low frequency filtering



Capacitors

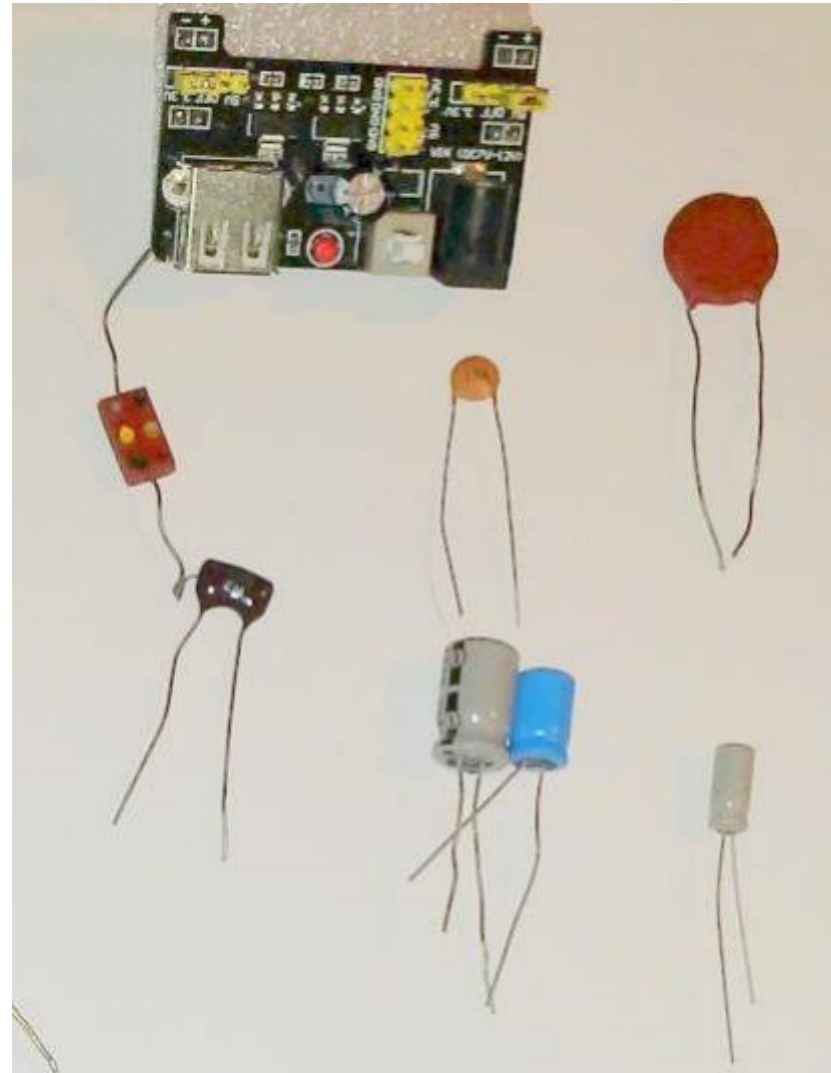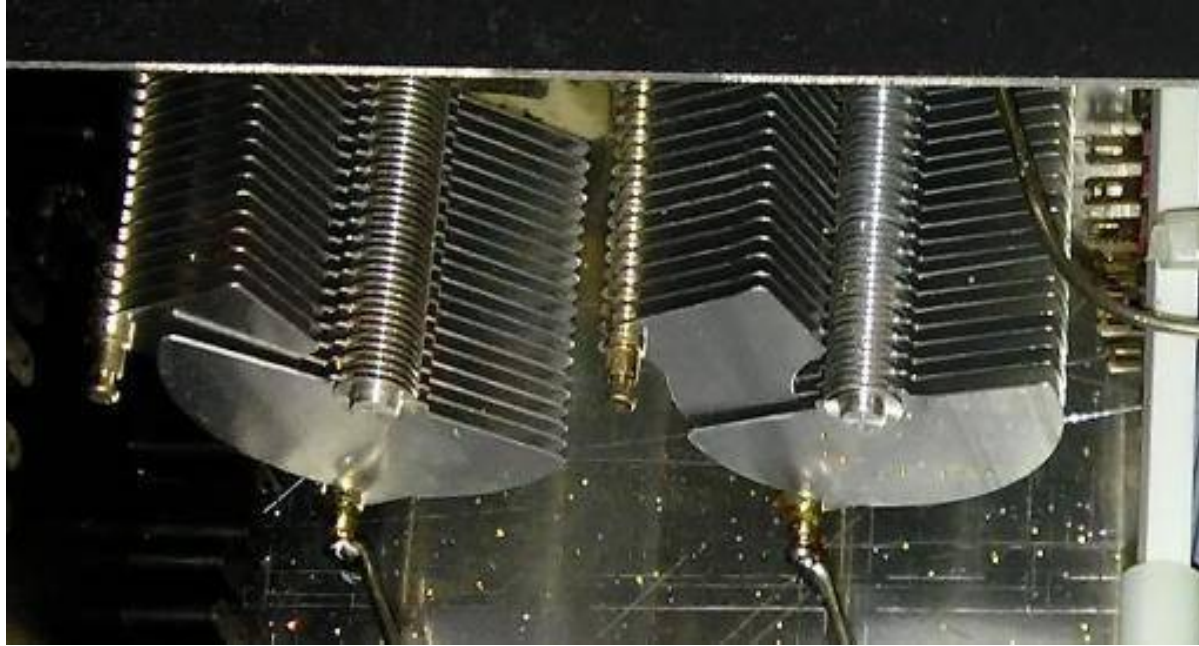


Inductors

- Air-core or iron-core
- Encapsulated (looks like resistor)
- Slug tuned (variable)
 - magnetic or non-magnetic core inside coiled inductor
 - Adjust with screw-driver

Inductors

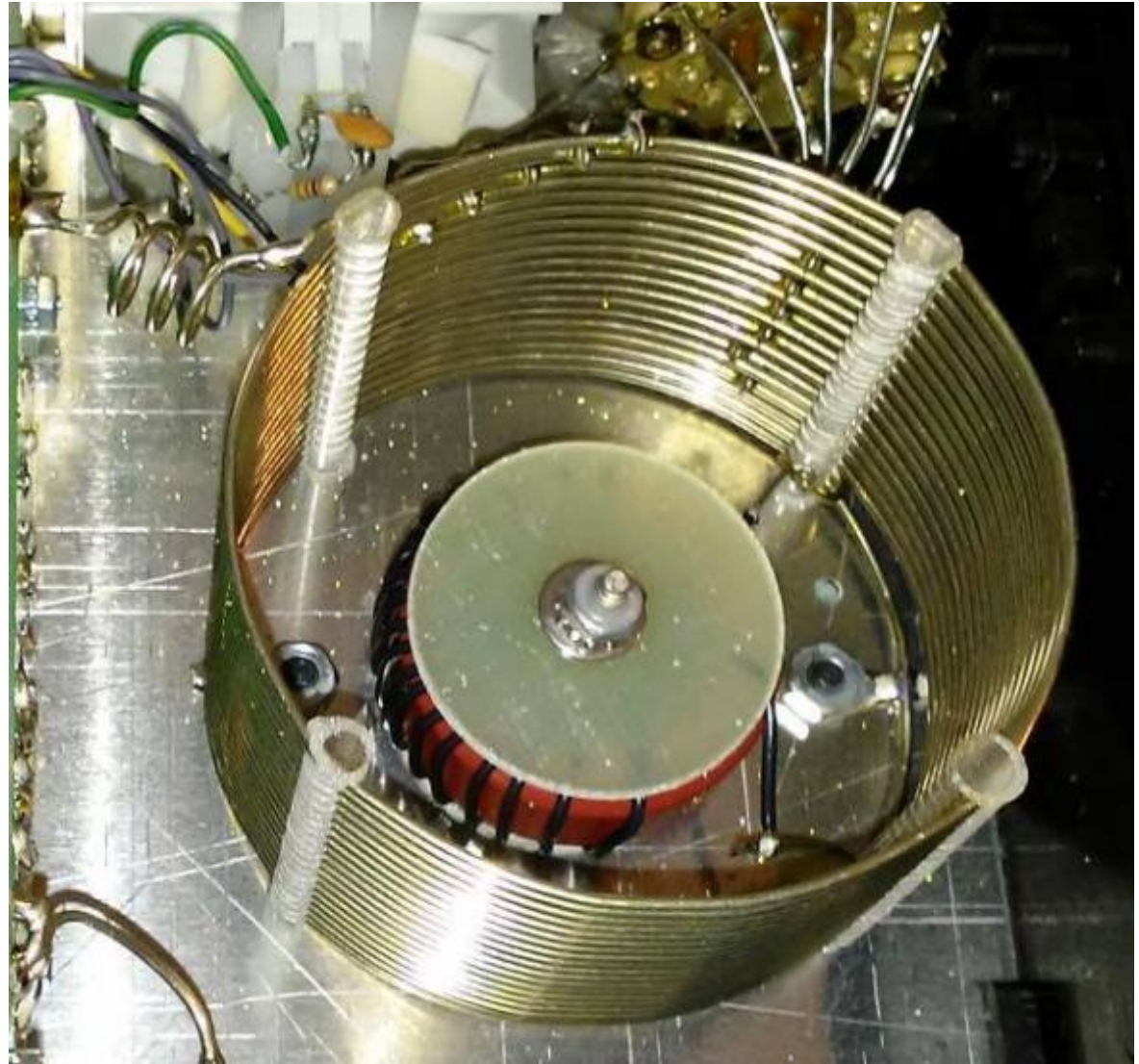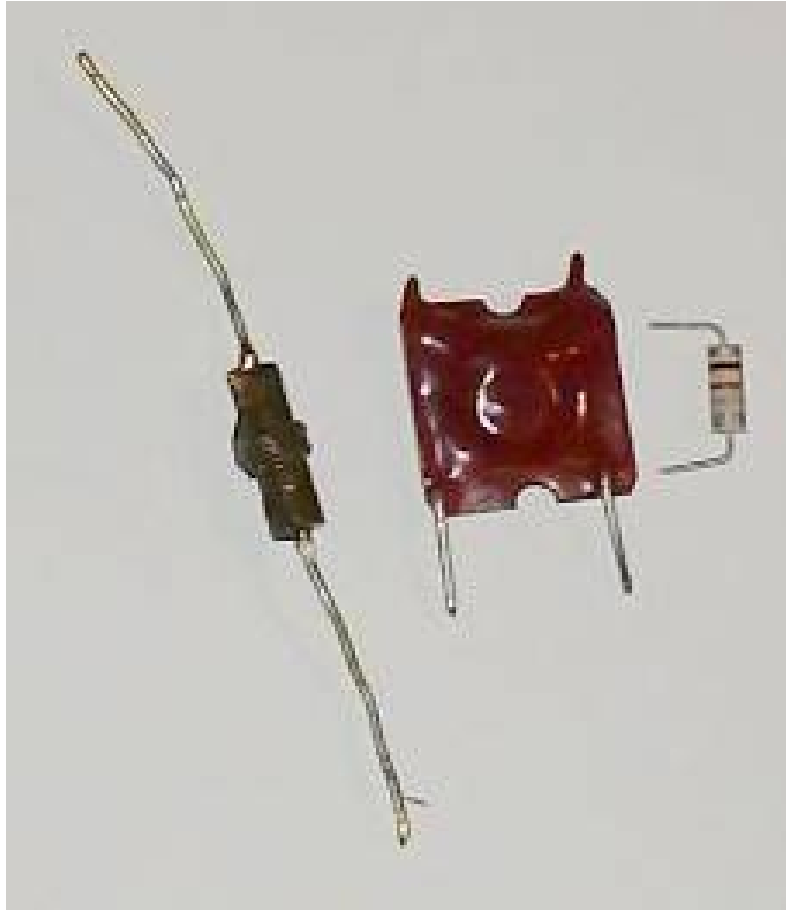


Transformers

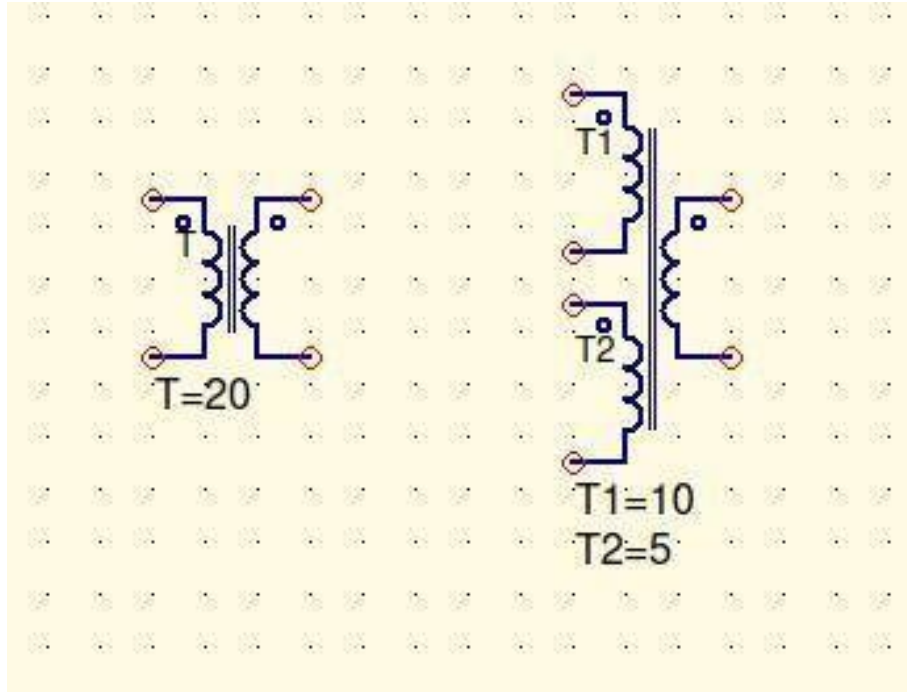

Switching Power Supply (Conceptual)

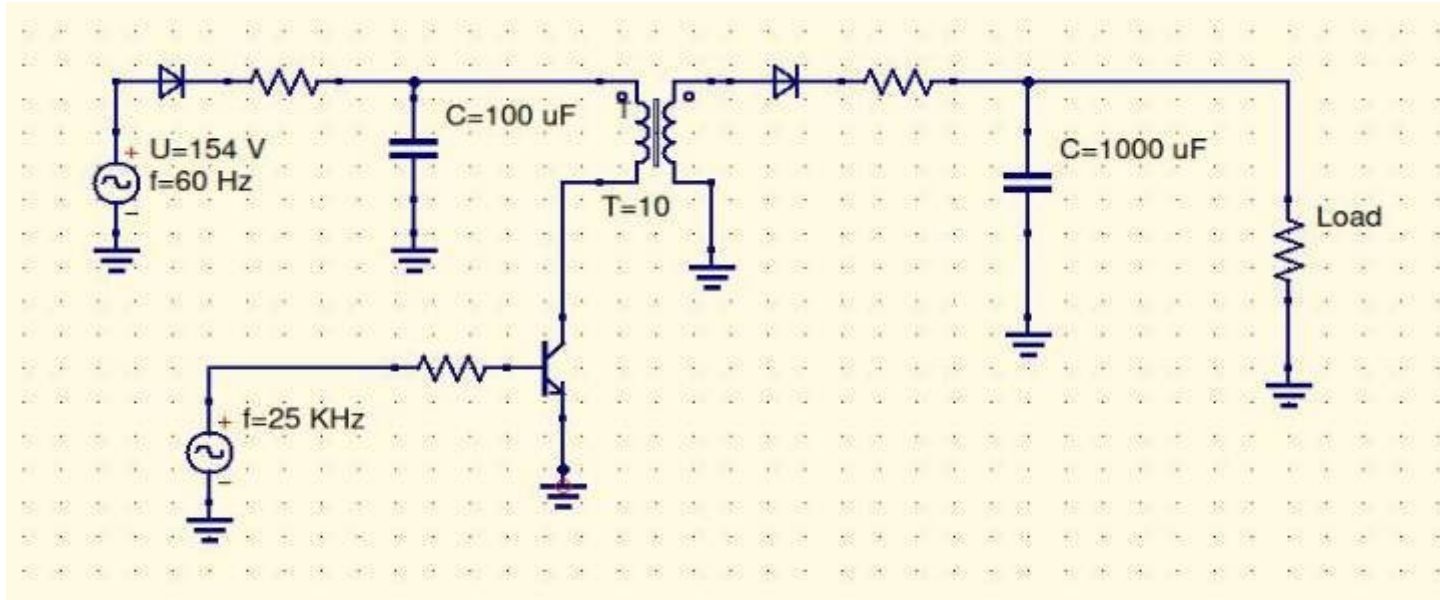- Use high frequency to minimize transformer size/weight
- Needs careful design/shielding to avoid HF interference



Semiconductors


- Diodes – Point Contact, Pin, Schottky, Varactor, Zener
 - Current, PIV, Speed, Reverse Current
- Transistors – BJT, JFET, MOSFET
 - Gain, Operating Regions and Parameters
- Optical – Photo, LED, Laser, Optoisolators

TOOLS


- Arduino UNO + Breadboard
- QUES – Quite Universal Circuit Simulator (Free)
 - <https://sourceforge.net/projects/qucs/files/latest/download>
- Circuit Calculations with Complex Numbers and Spreadsheets (Excel or LibreOffice CALC)
 - Free LibreOffice Download: <https://www.libreoffice.org/>

Arduino and Breadboard

CQ CQ DE AE7OH K

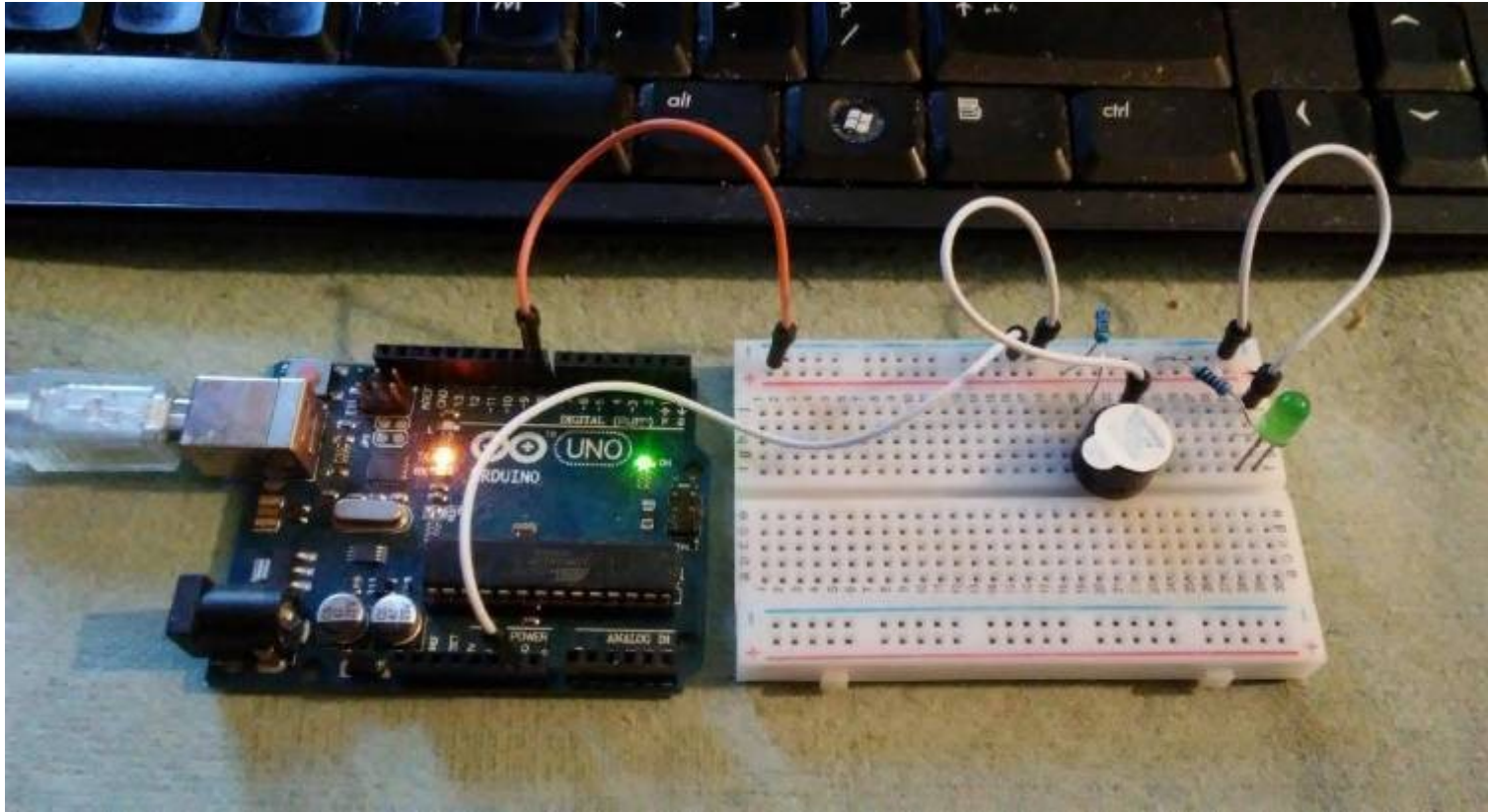


Arduino+Breadboard Schematic

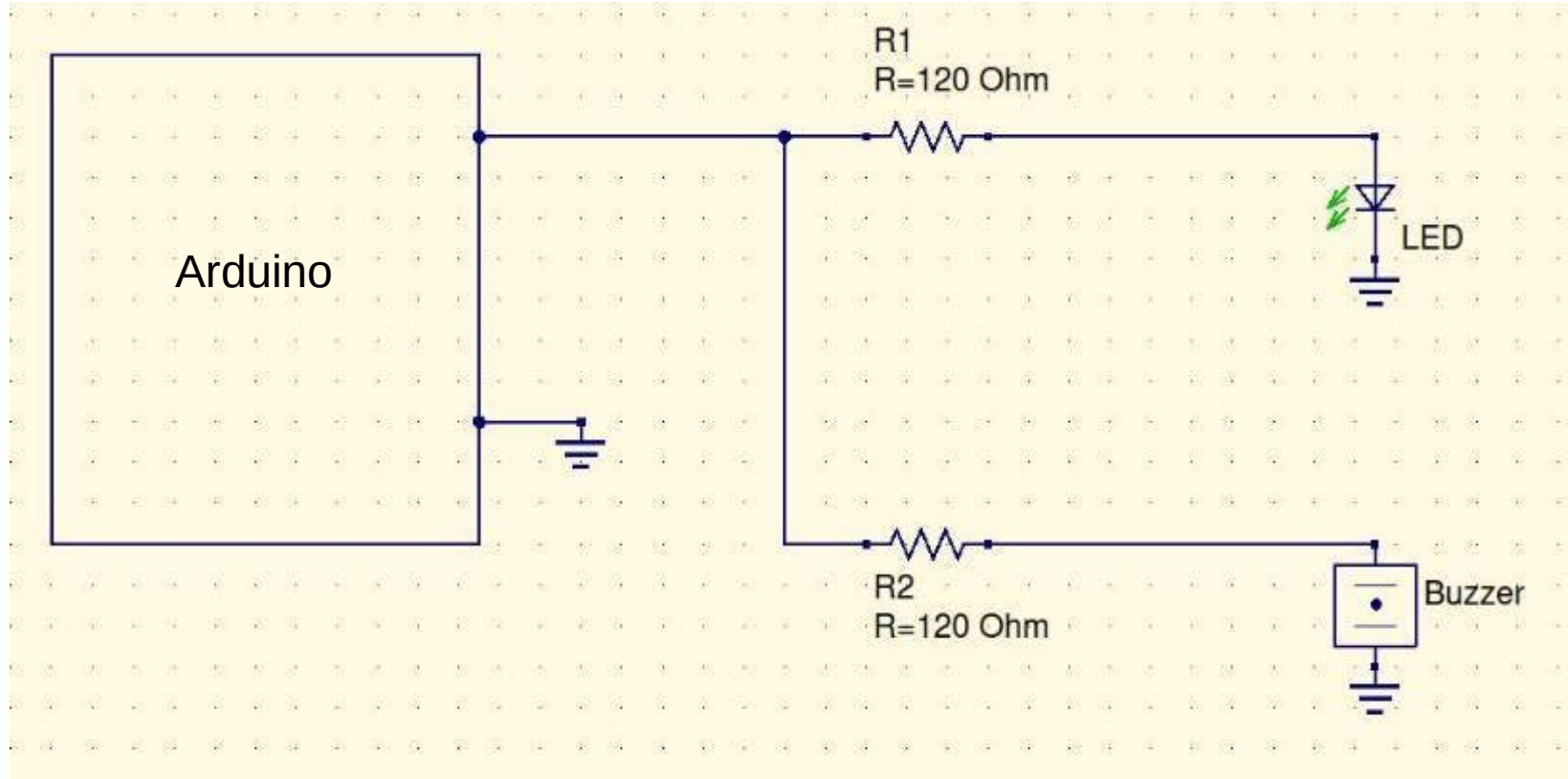









Quite Universal Circuit Simulator

<https://sourceforge.net/projects/qucs/files/latest/download>

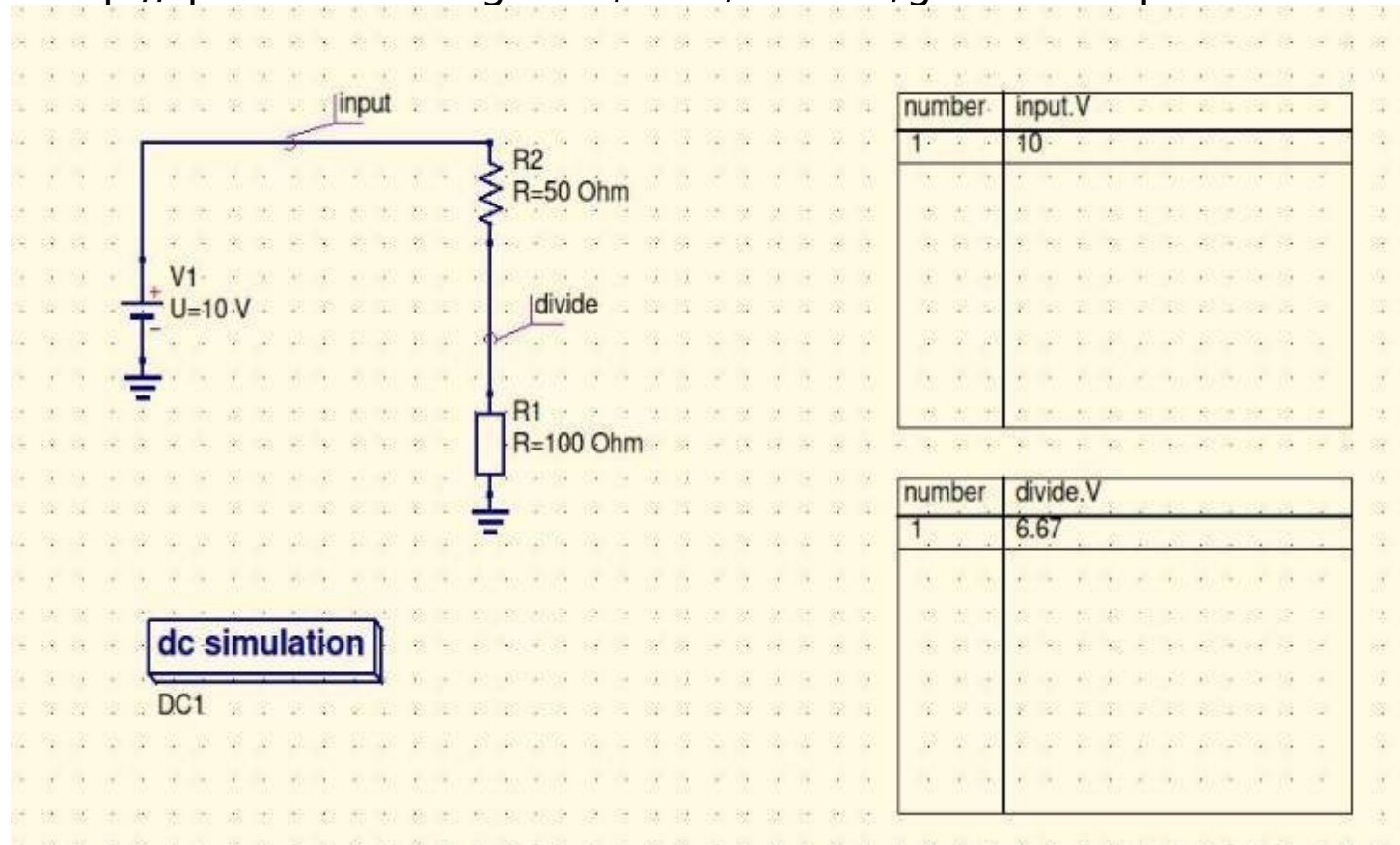Manual: <http://qucs.sourceforge.net/docs/tutorial/getstarted.pdf>




Some Semiconductor Symbols

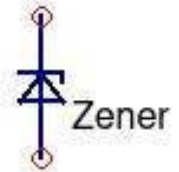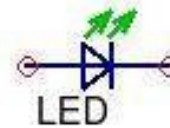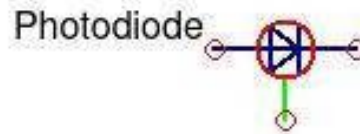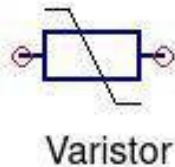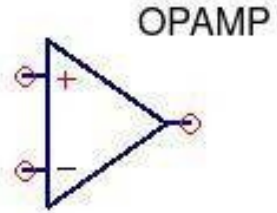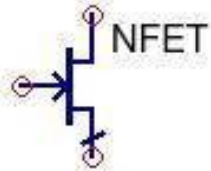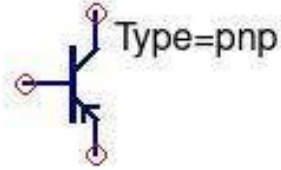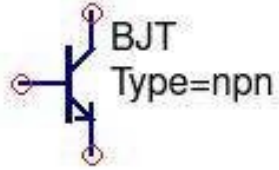



RLC Transient Simulation

transient
simulation


TR1
Type=lin
Start=0
Stop=10 ms

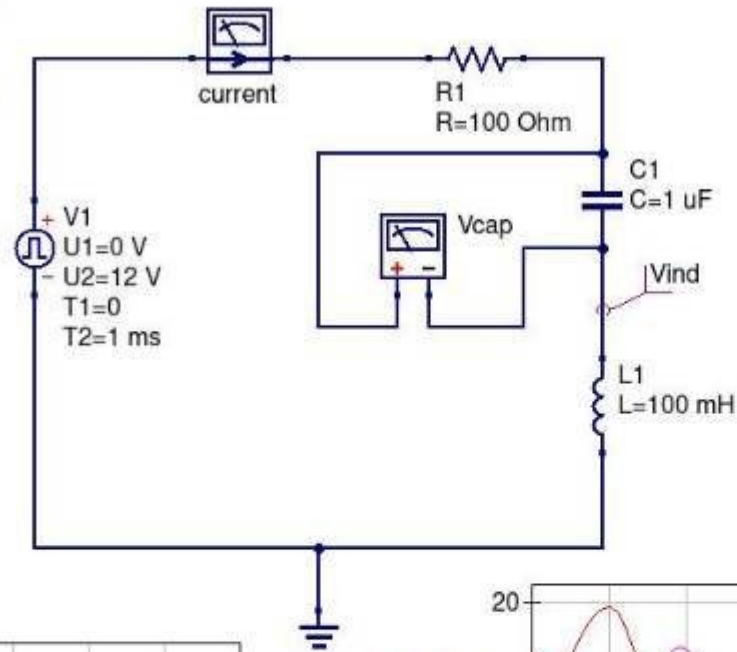

time	current.It	Vcap.Vt	Vind.Vt
0	0	0	0
0.000101	0.0113	0.587	10.3
0.000202	0.0205	2.21	7.74
0.000303	0.0268	4.63	4.69
0.000404	0.0299	7.52	1.49
0.000505	0.0299	10.6	-1.55
0.000606	0.0269	13.5	-4.15
0.000707	0.0217	15.9	-6.1
0.000808	0.0149	17.8	-7.27
0.000909	0.00729	18.9	-7.64
0.00101	-0.000903	19.3	-19.2
0.00111	-0.019	18.2	-16.3
0.00121	-0.0335	15.5	-12.2
0.00131	-0.0433	11.6	-7.29
0.00141	-0.0481	6.97	-2.16
0.00152	-0.0478	2.09	2.69
0.00162	-0.0429	-2.53	6.82

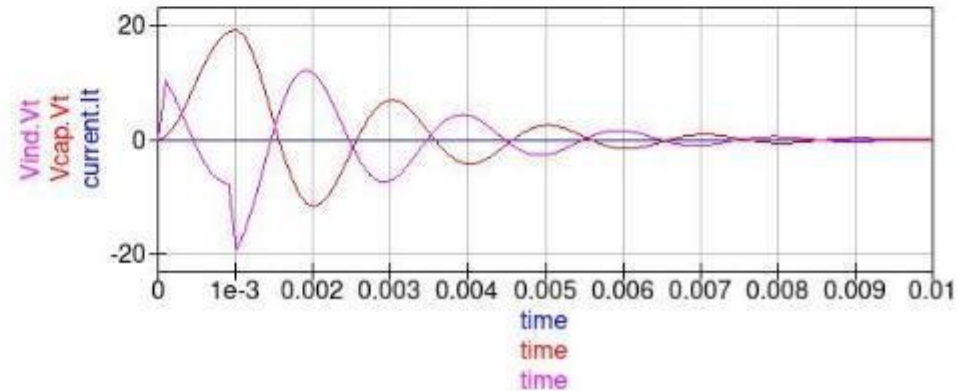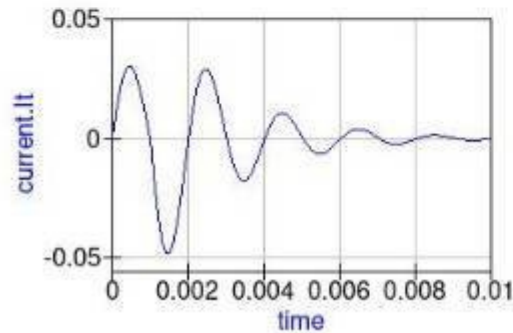

RLC Frequency And Transient Simulations


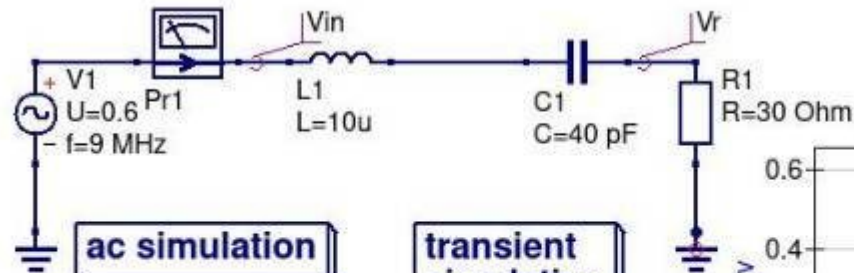


ac simulation


AC1
Type=lin
Start=4 MHz
Stop=12 MHz
Points=1001

transient simulation

TR1
Type=lin
Start=0
Stop=5 us

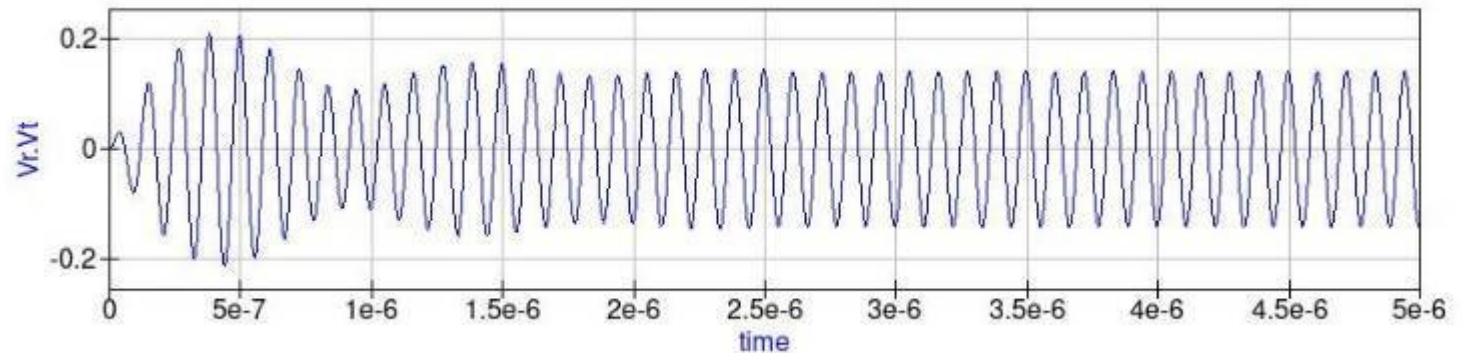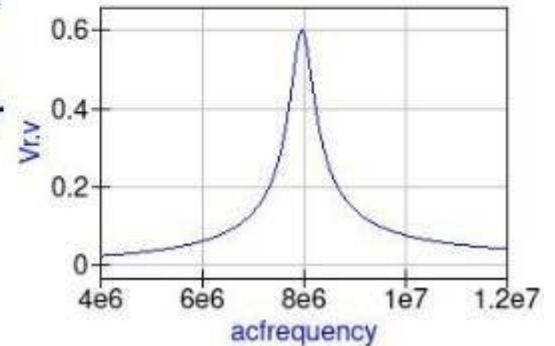





Simple Power Supply

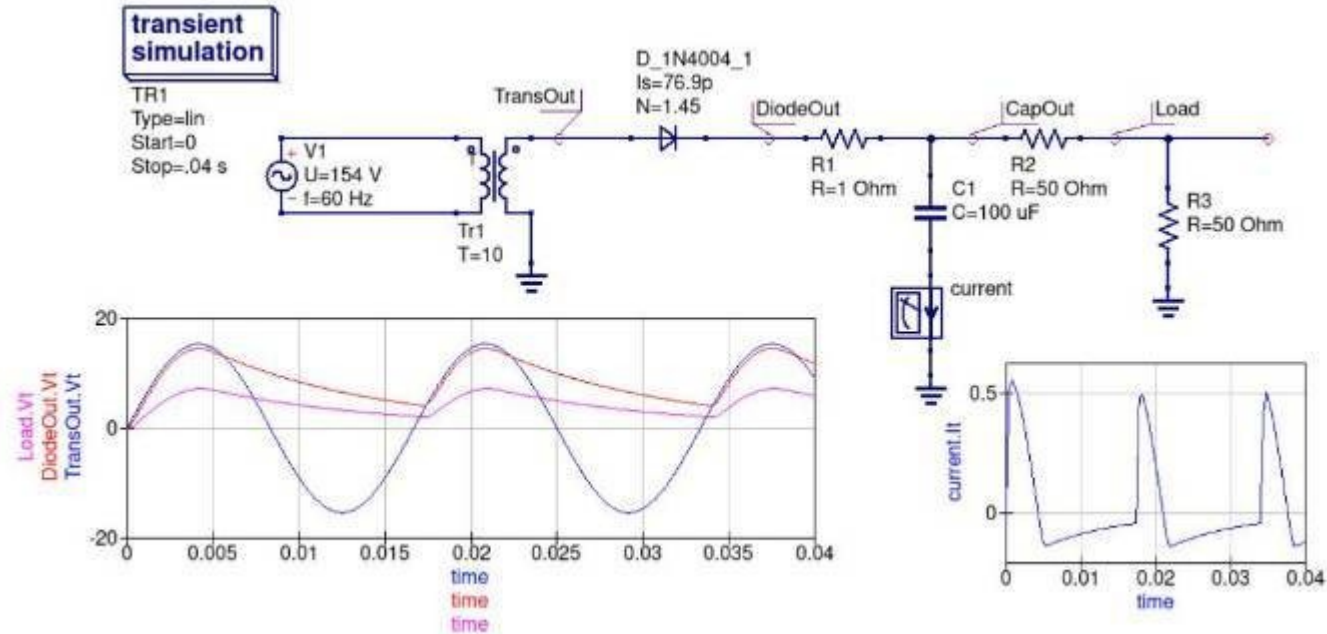



Regulated Power Supply

**transient
simulation**

TR1
Type=lin
Start=0
Stop=.05 s

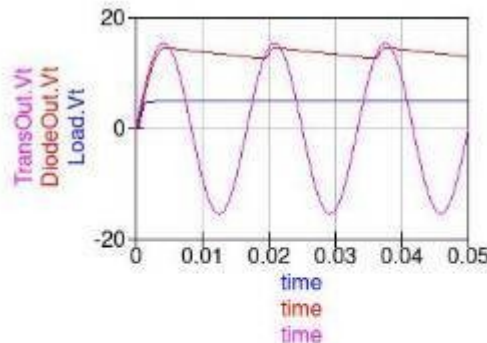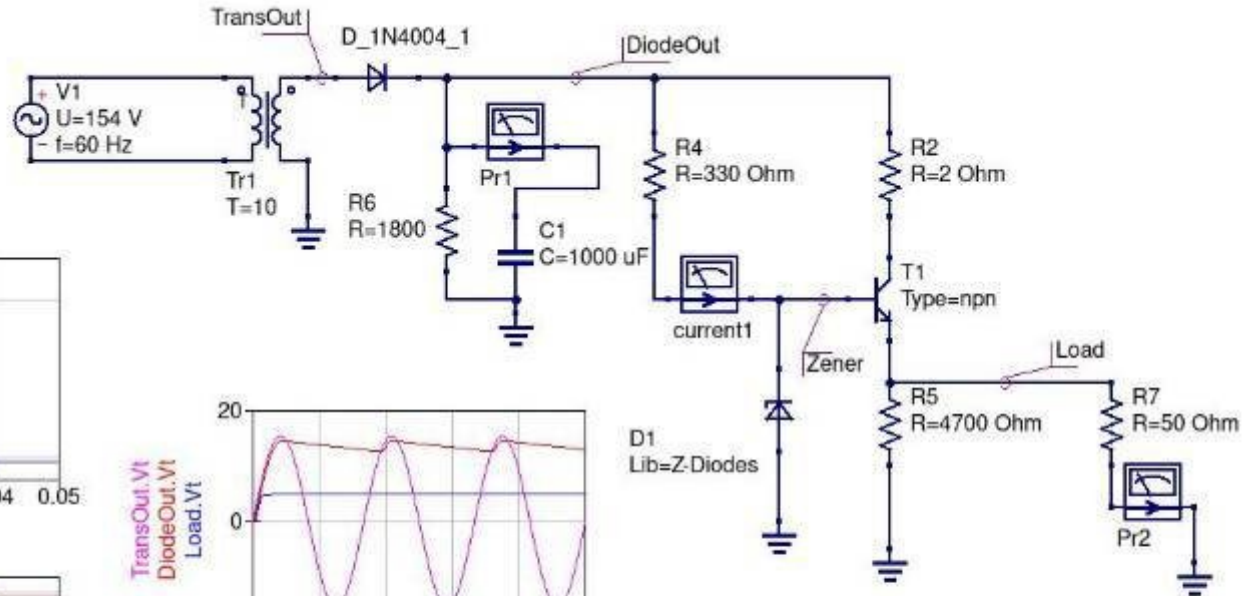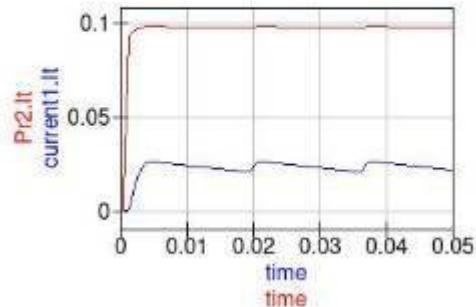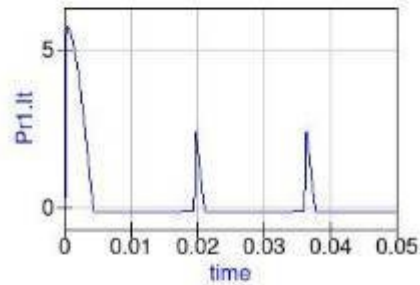

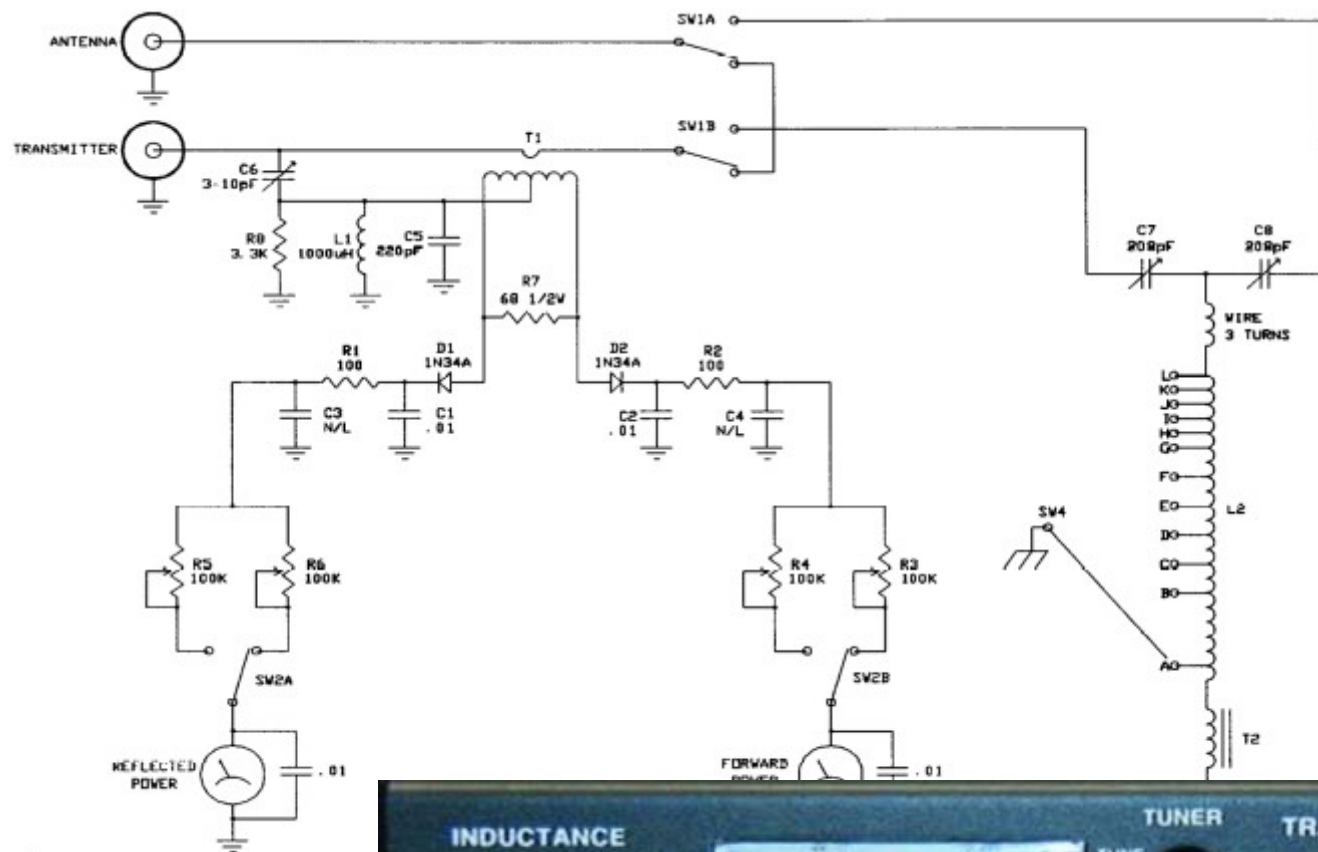


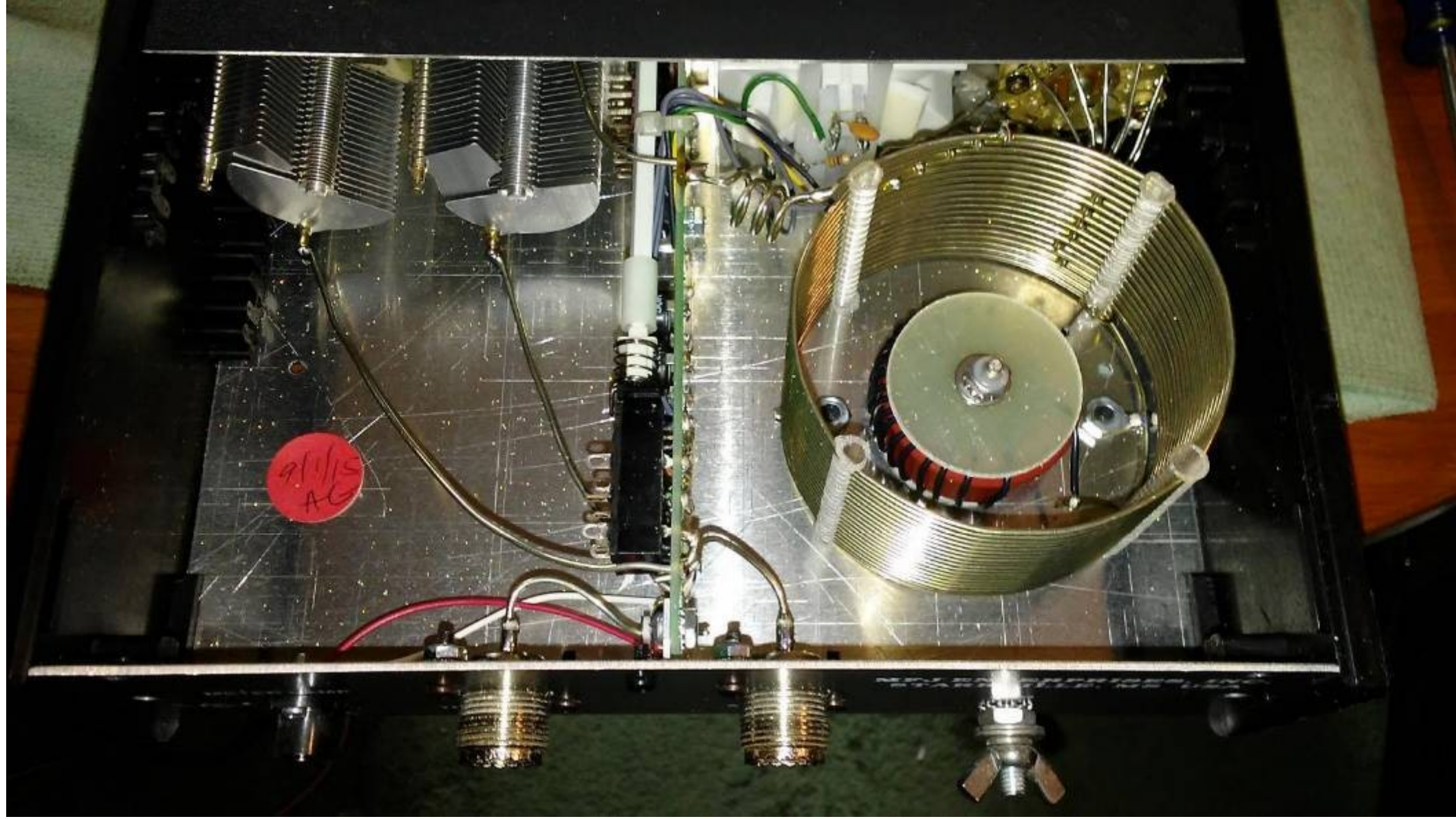


Alternating Current Sine Waves

Radial rotates at f cycles per second
to create a sine wave

Imaginary axis
(j or i)

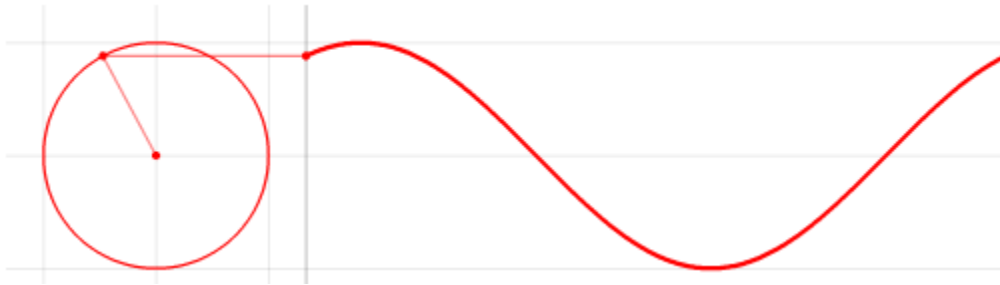


Real
axis

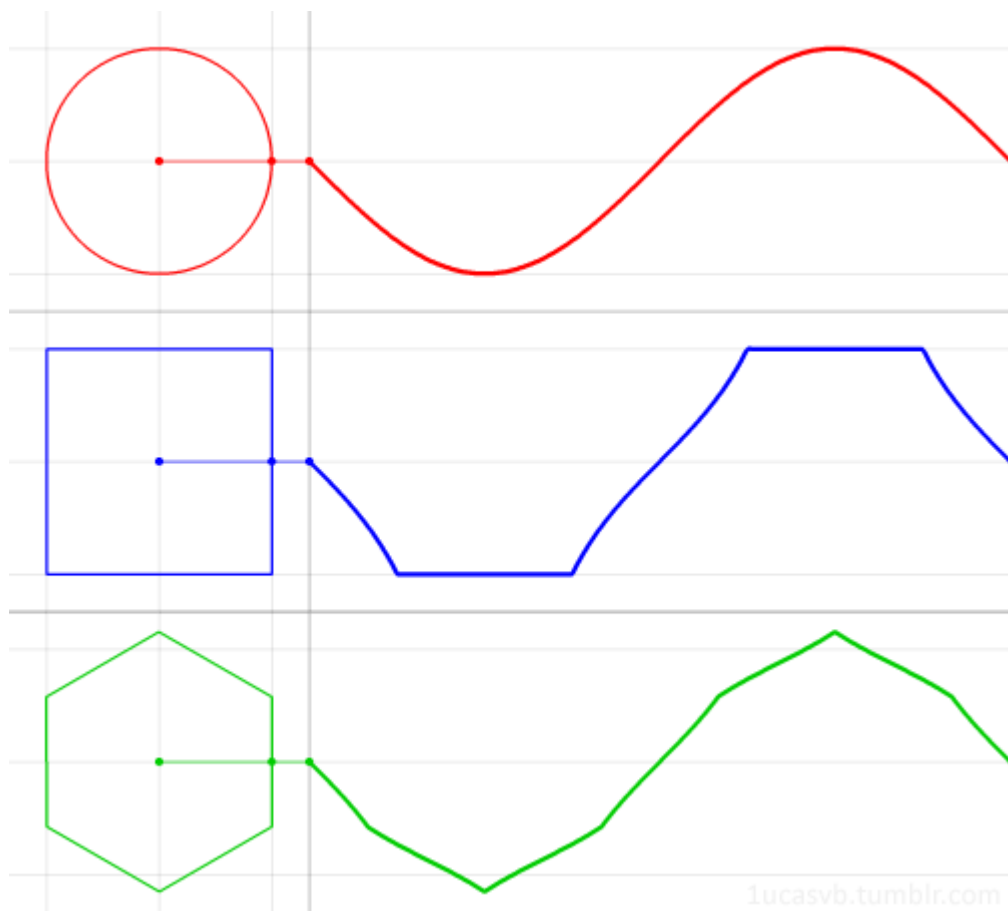


AC Representations


Vectors

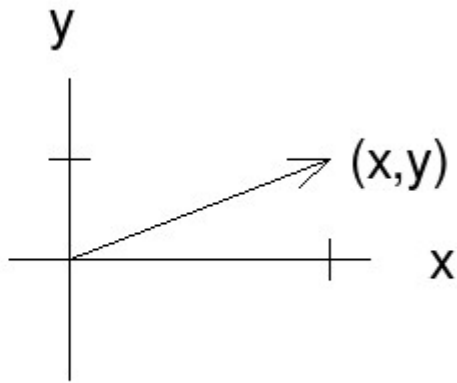


Polar Form

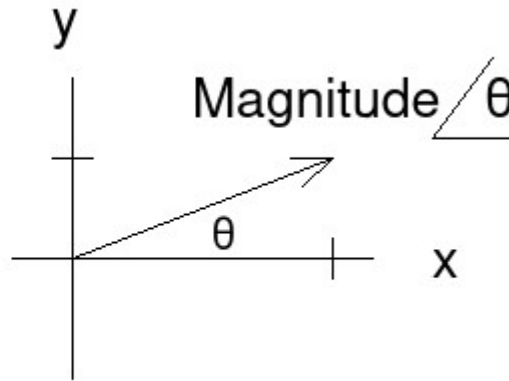

Complex Numbers (easy calculations)

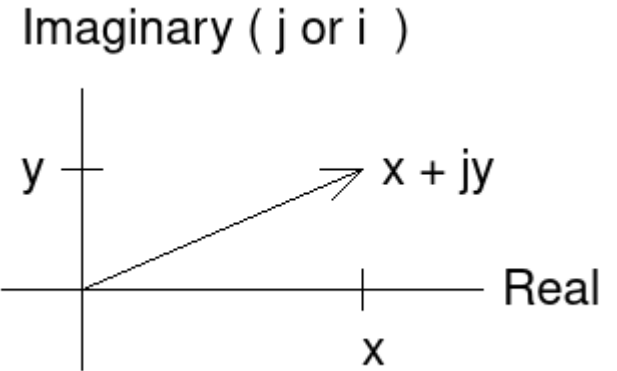

Calculate Impedance Match

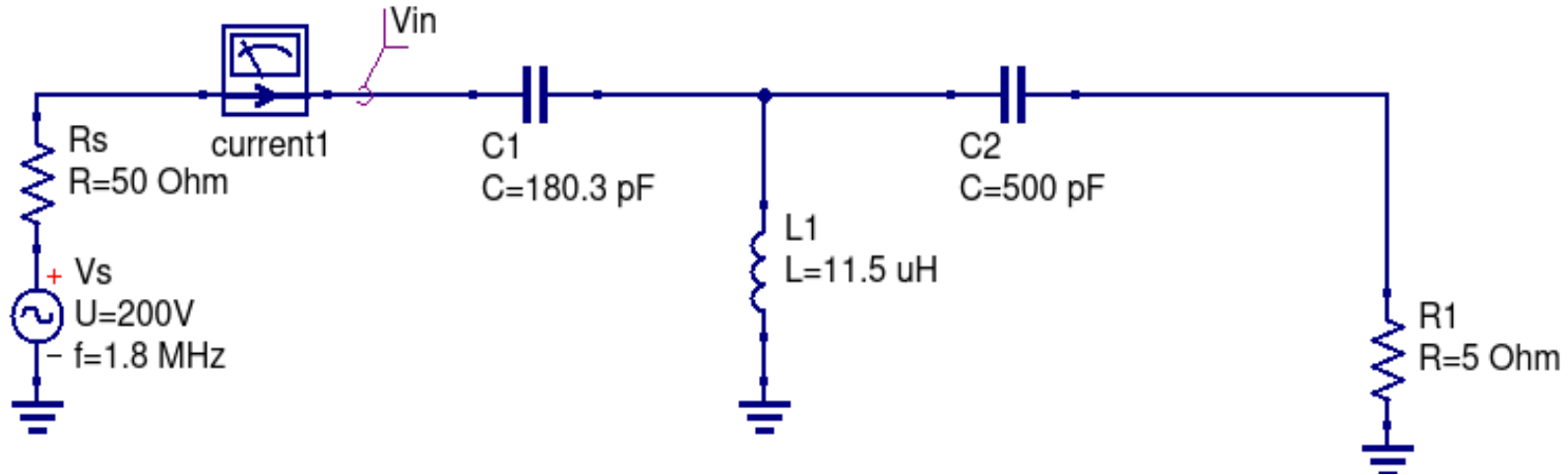

$$\frac{1}{j\omega C1} + \frac{1}{\frac{1}{j\omega L1} + \frac{1}{R1 + \frac{1}{j\omega C2}}}$$

Impedance Match Calc Spreadsheet

(See Figure 24.4 in Antenna Book)

	A	B	C	D	E	F	G	H	I
1				T NETWORK			ANTENNA/LOAD		
2	component		C-xmtr		C-antenna		x	y	
3				L					
4									
5									
6	value		1.80E-10	1.15E-05	5.00E-10		5	0	
7			(180.3 pf)	(11.5 uhenry)	(500 pf)				
8									
9	reactance		-490.402038344852i	130.061826i	-176.838975027154i		5		
10									
11									
12	(1.8 Mhz)	freq	1.80E+06			38.2180330964639-2.79408640923299i			
13	radian_freq	rad. Freq.	11309724			answer			
14									
15									
16		Q	1000	200	1000				
17			0.490402038344852-490.402038344852i	0.65030913+130.061826i	0.176838975027154-176.838975027154i		5		
18									
19									
20						49.0615676552388-4.68763200560596i			
21						answer			
22									
23									


=IMSUM(C9,IMDIV(1,IMSUM(IMDIV(1,D9),IMDIV(1,IMSUM(E9,G9))))))

Excel or CALC Complex Functions


COMPLEX	Returns a complex number, given real and imaginary parts as numbers.	IMLOG10	Returns the base-10 logarithm of a complex number.
IMABS	Returns the absolute value of a complex number.	IMLOG2	Returns the base-2 logarithm of a complex number.
IMAGINARY	Returns the imaginary part of a complex number.	IMPOWER	Returns a complex number raised to a power.
IMARGUMENT	Returns the argument of a complex number.	IMPRODUCT	Returns the product of complex numbers.
IMCONJUGATE	Returns the complex conjugate of a complex number.	IMREAL	Returns the real part of a complex number.
IMCOS	Returns the cosine of a complex number.	IMSEC	Returns the secant of a complex number.
IMCOSH	Returns the hyperbolic cosine of a complex number.	IMSECH	Returns the hyperbolic secant of a complex number.
IMCSC	Returns the cosecant of a complex number.	IMSIN	Returns the sine of a complex number.
IMCSCH	Returns the hyperbolic cosecant of a complex number.	IMSINH	Returns the hyperbolic sine of a complex number.
IMCOT	Returns the cotangent of a complex number.	IMSQRT	Returns the square root of a complex number.
IMDIV	Returns the result of dividing one complex number by another.	IMSUB	Returns the difference between 2 complex numbers.
IMEXP	Returns e to the power of a complex number.	IMSUM	Returns the sum of complex numbers.
IMLN	Returns the natural logarithm of a complex number.	IMTAN	Returns the tangent of a complex number.

Adjustments for Component Q

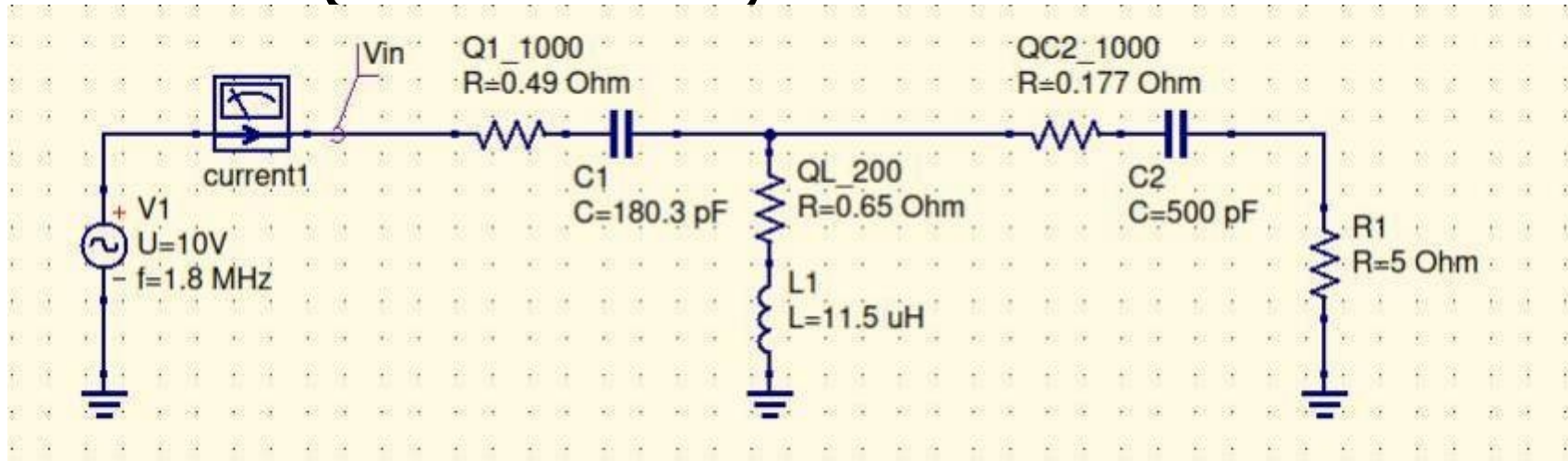- Match adjusted 5-Ohm Antenna to 38 ohms
- Ant. Book assumed Q-values for components
- Added Q-Resistors yield 50 ohms




Match

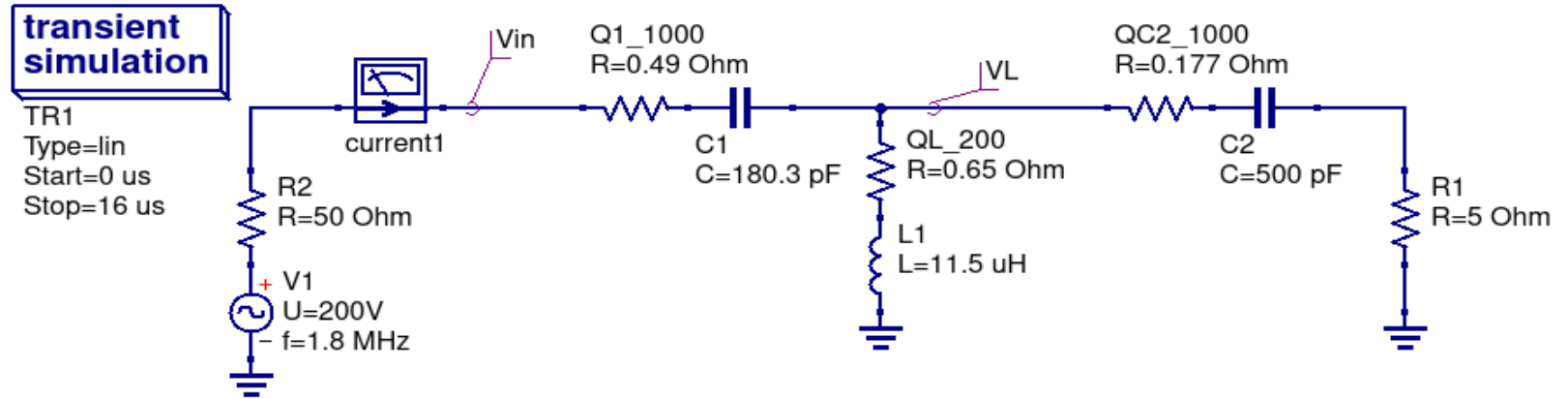

Input voltage: 100V

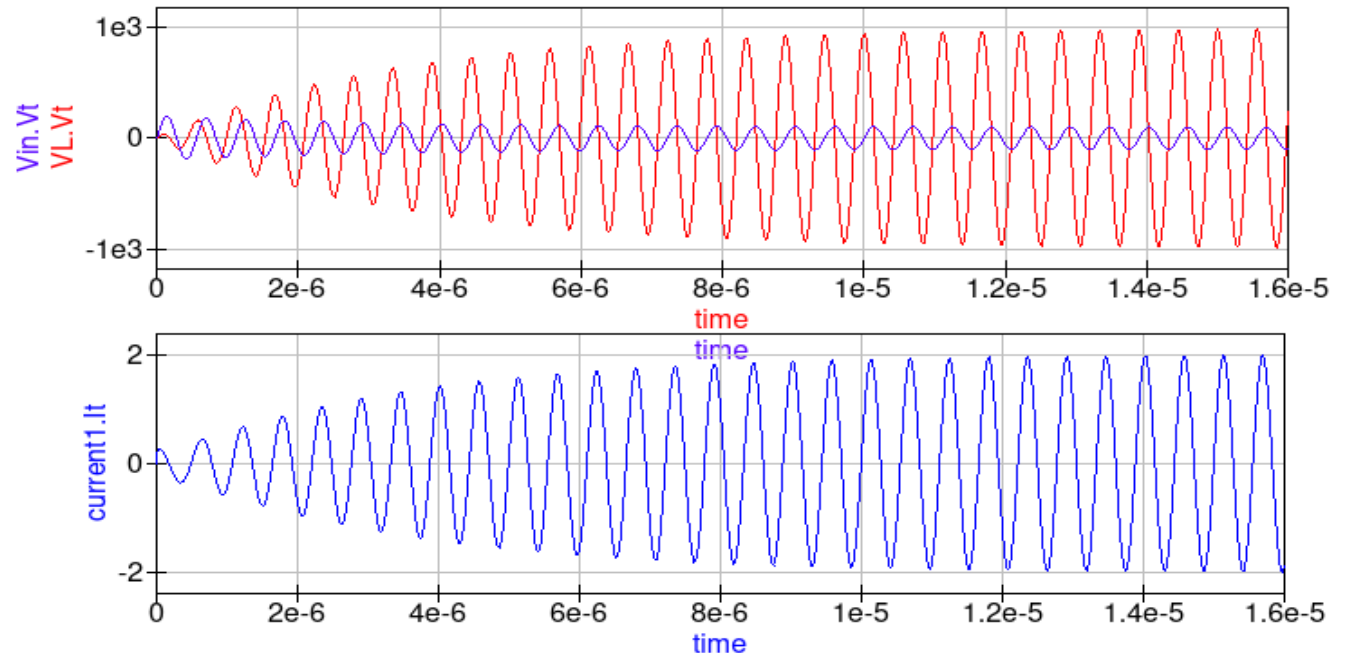But peak
voltages
across tuner
elements are
1000V




High RF Tuner Voltages

- High Voltage in tuner elements
 - 100 volts peak source
 - 1000 volts peak across components
- Arcing and RF burns potential
- Solutions include better antenna design
 - e.g., a Balun can help match



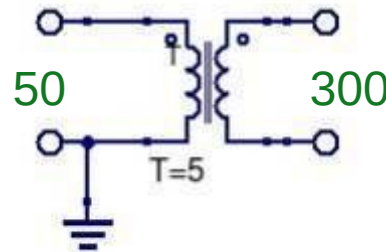Example: 5:1 transformer
Matches 50 ohm coax
To 300 ohm antenna






HAM Radio Board of Education
NEVER STOP LEARNING

Questions?

You may email questions later to
phil.brunner@gmail.com

SDR - Software Defined Radio

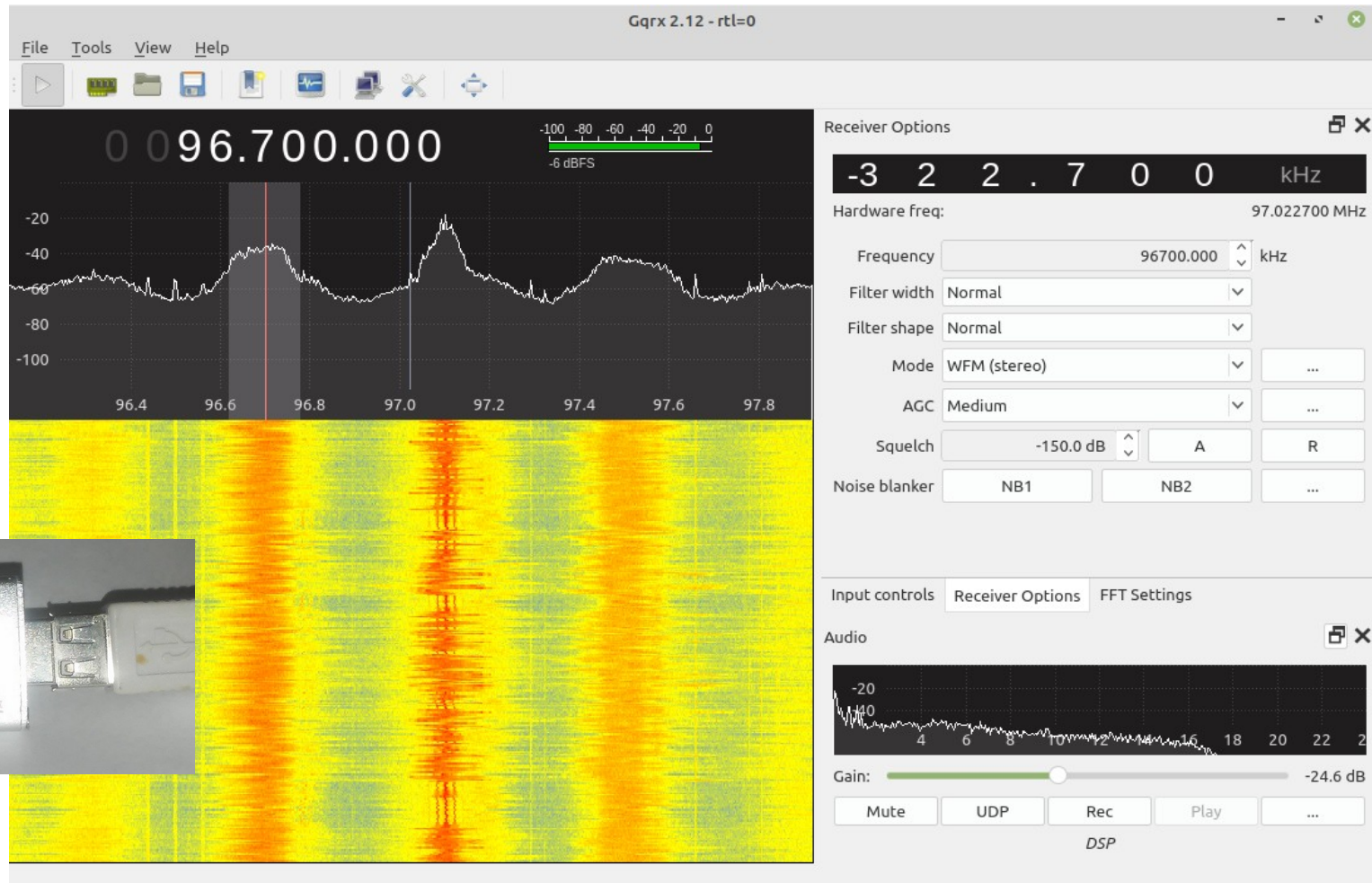

GQRX (Linux, etc.) <https://gqrx.dk/download>
SDR# (Windows) <https://airspy.com/download/>