



HAM Radio Board of Education
NEVER STOP LEARNING

Antenna Summit

Sponsored by



Session 3 – Components

Chapter 4.1 to 4.5.6

+ Other Material



Instructor:

Phil Brunner – AE7OH (was K9DTD, W6GOL)

- ARRL HANDBOOK for Radio Communications
- – (Reference for detailed information)
- Q & A via Chat or at the end of each hour
- Email questions to: phil.brunner@gmail.com
- Viewgraphs are at <http://HamRadioEdu.com>

Chapter 4 – Components

- The World of electronics is changing rapidly
 - Landlines replaced by Cell Phone, Zoom, Skype
 - Vacuum Tubes Disappearing – (Light Bulbs, CRTs, Radio Tubes)
- Computers and DSPs are replacing individual components and units.
- Software Defined Radios are available today.
- We will concentrate on characteristics and skip the details!

Components Characteristics

- Practical Resistors, Capacitors and Inductors
 - Transformers
 - Semiconductors
 - Amplifiers
 - Vacuum Tubes
-
- Circuit Simulation and Analysis Tools
 - Antennas and Tuners
 - Software Defined Radios and Units

Starting Big - 112-foot



112-foot Goldstone
Deep Space
Antenna
with Subreflector

Satellite Antennas


Defense Support Program

https://en.wikipedia.org/wiki/Defense_Support_Program



Chandra X-ray Telescope

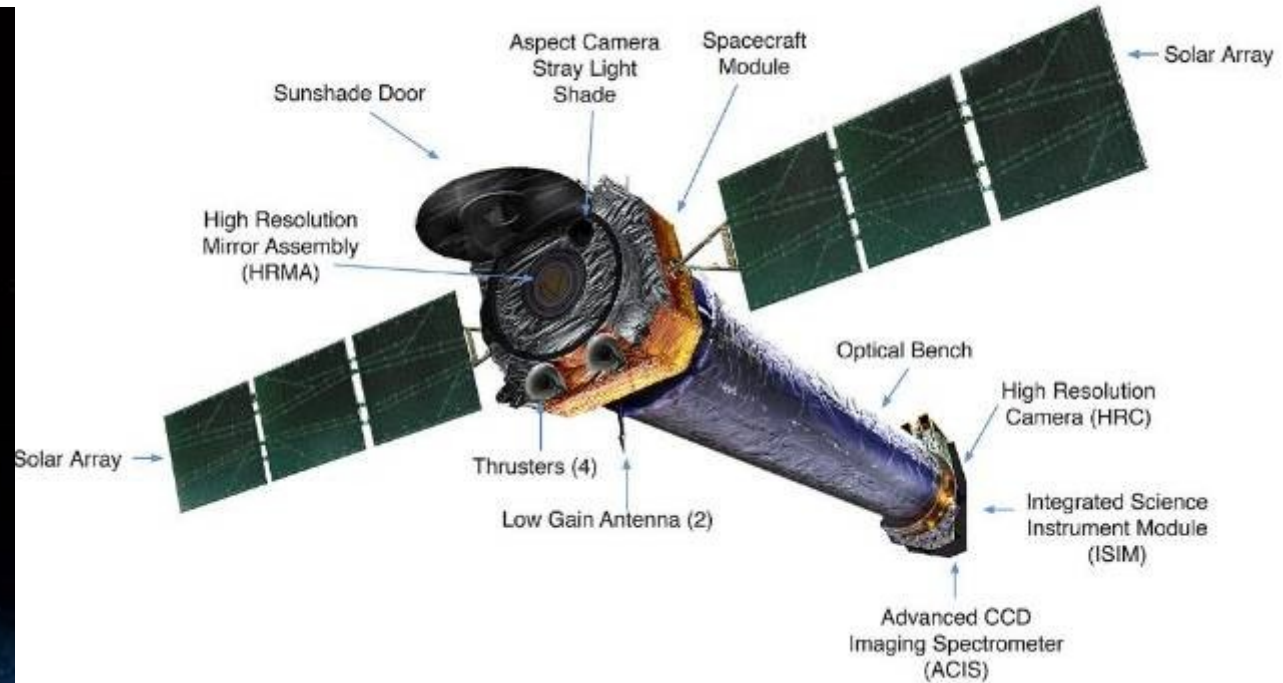
https://en.wikipedia.org/wiki/Chandra_X-ray_Observatory



Resistors

- Wire size suitable for max current
- Resistance usually increases with temperature
- Component Resistors
 - Carbon, Metal-oxide
 - Wirewound- low-frequency due to inductance
 - Metal-film, Carbon-film – deposit on insulating substrate
- Power rating and temperature stability are considerations
- Tolerance often unimportant – 20%, 10%, 5%, 1%
- Potentiometers – variable resistors



Resistors

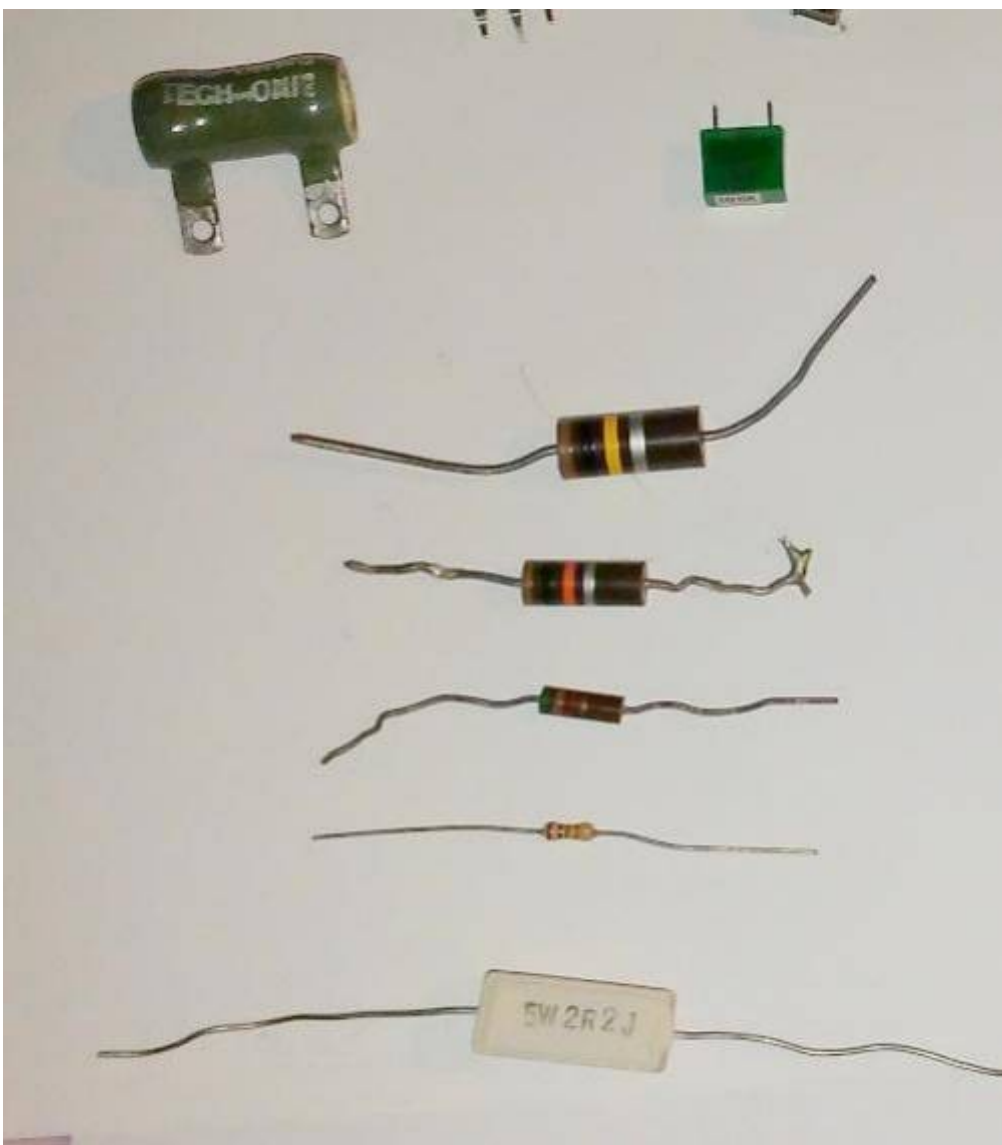

Capacitors

- Ideally blocks DC, no leakage, no energy loss
- Tolerance and temperature coefficient
- Voltage rating and breakdown
- Frequency, resistance, leakage, inductance considerations
- Ceramic, plastic film, mica, electrolytic, air-variable, vacuum
- Electrolytics are high capacity and polarized - low frequency filtering



Capacitors

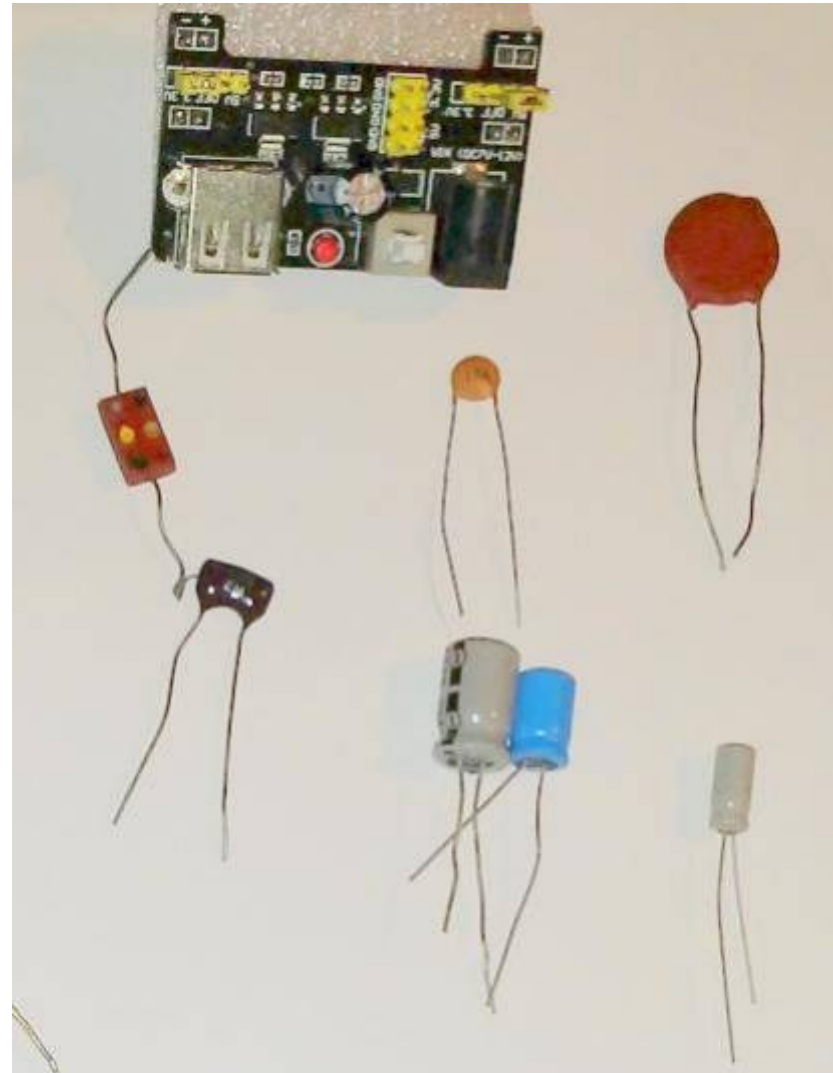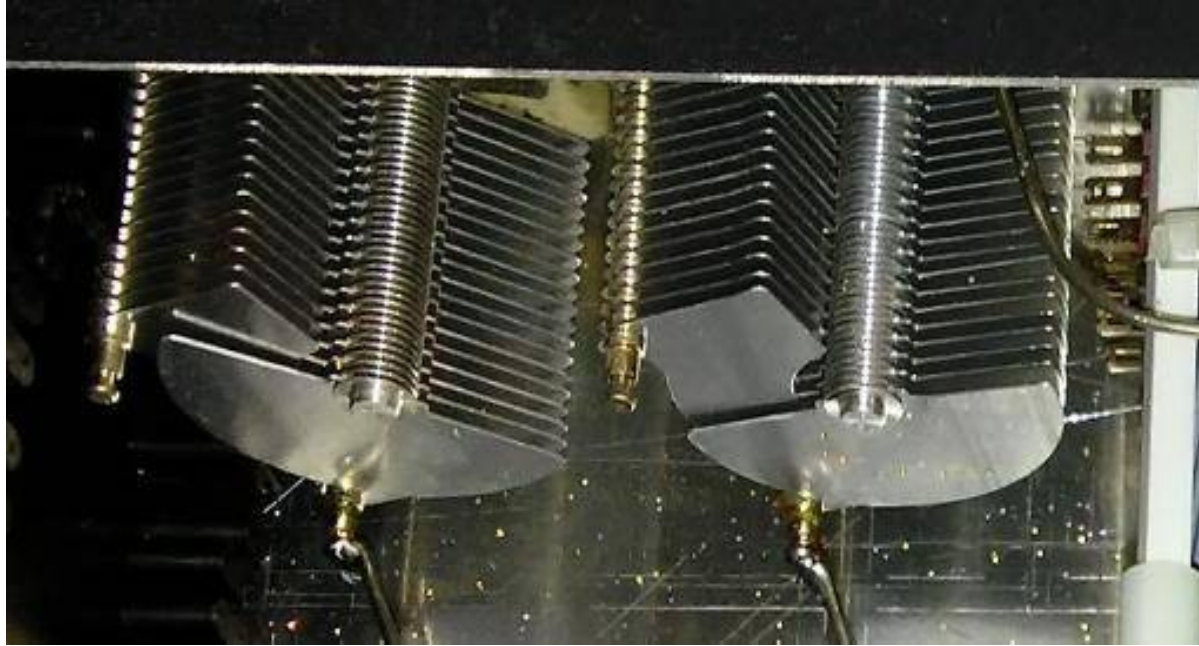


Inductors

- Air-core or iron-core
- Encapsulated (looks like resistor)
- Slug tuned (variable)
 - magnetic or non-magnetic core inside coiled inductor
 - Adjust with screw-driver

Inductors

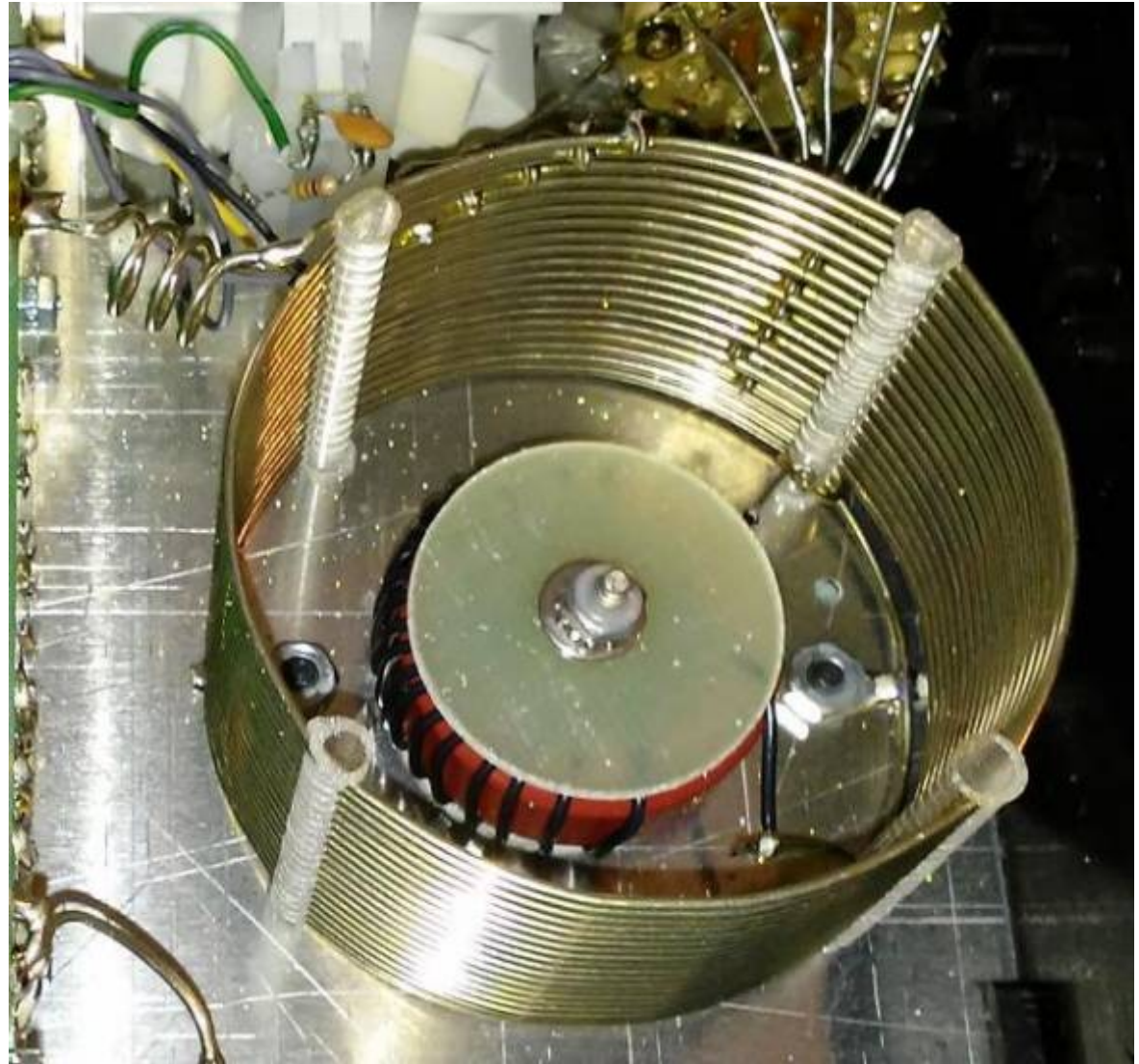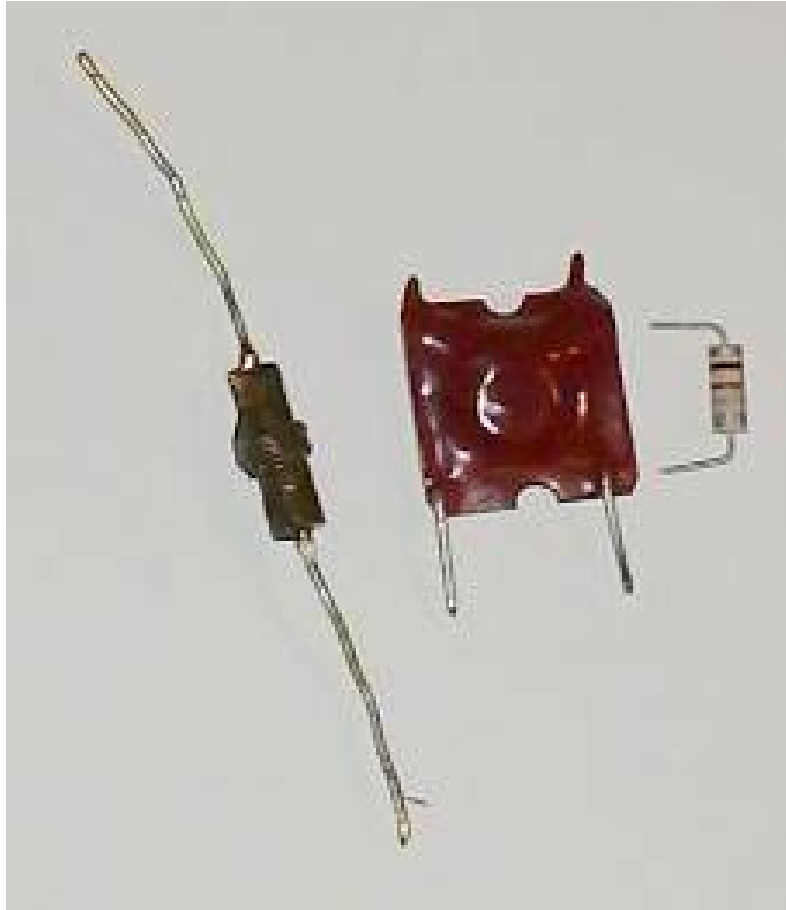


Transformers

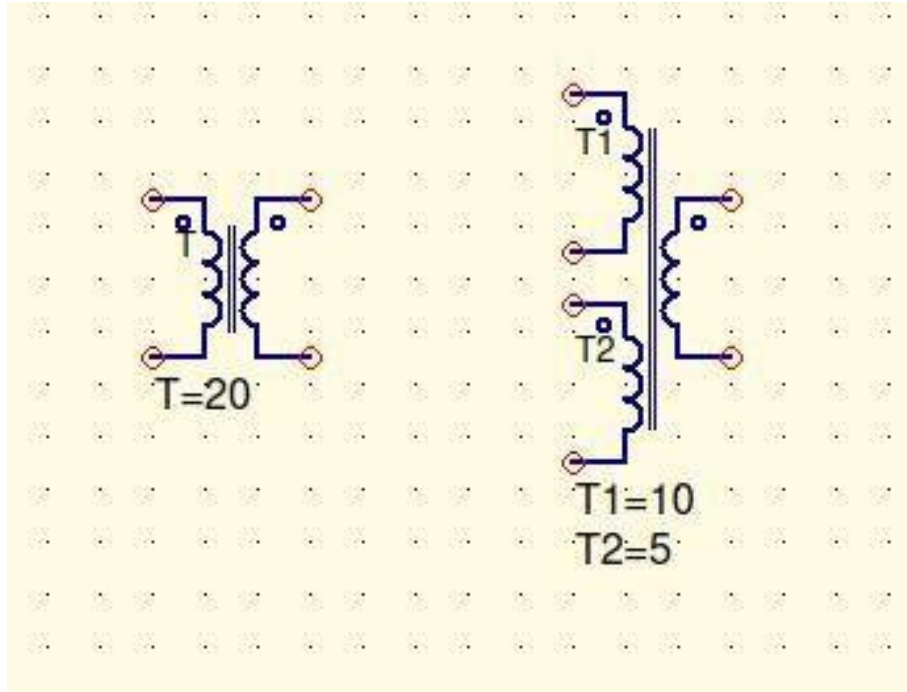

Switching Power Supply (Conceptual)








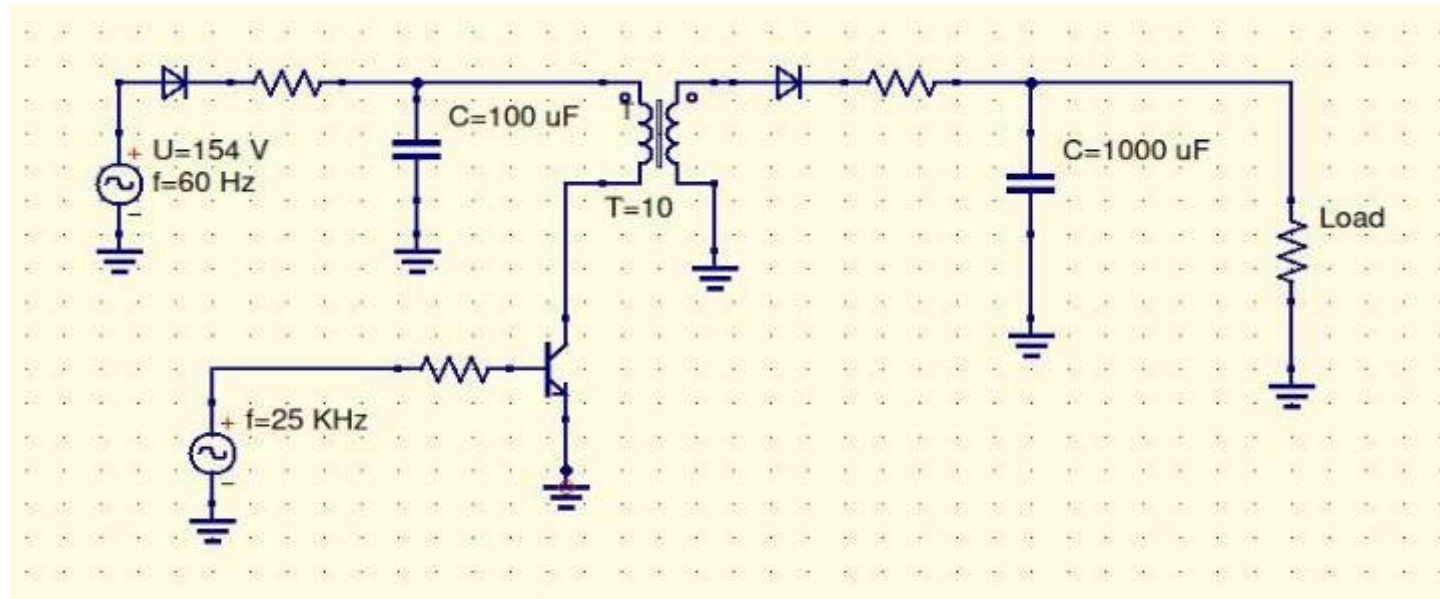
- Use high frequency to minimize transformer size/weight
- Needs careful design/shielding to avoid HF interference






Semiconductors

- Diodes – Point Contact, Pin, Schottky, Varactor, Zener
 - Current, PIV, Speed, Reverse Current
- Transistors – BJT, JFET, MOSFET
 - Gain, Operating Regions and Parameters
- Optical – Photo, LED, Laser, Optoisolators
- Fiber Optics

Some Semiconductor Symbols

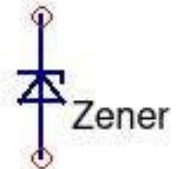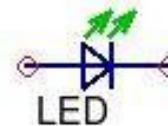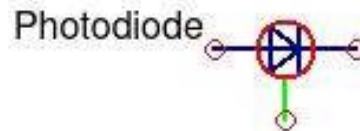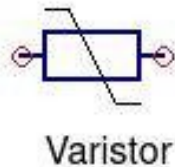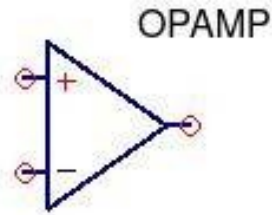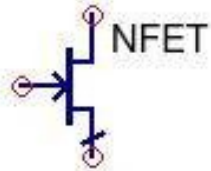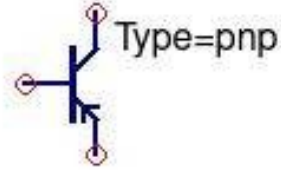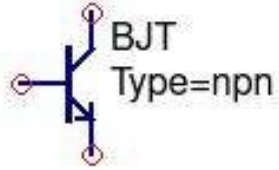

NPN Amplifier

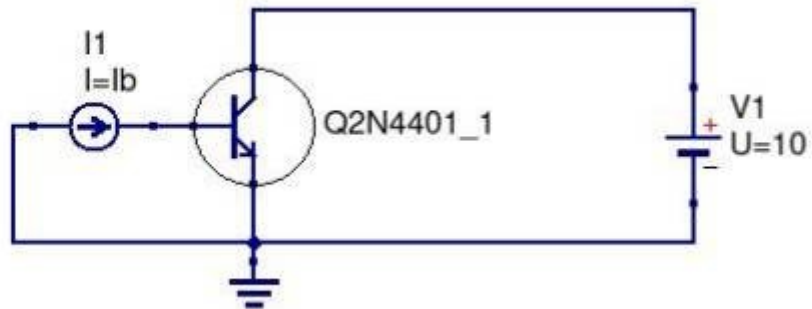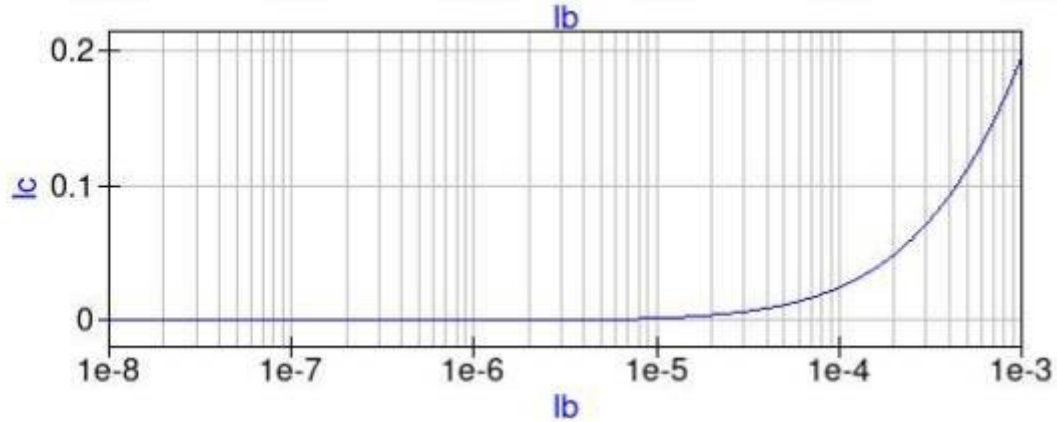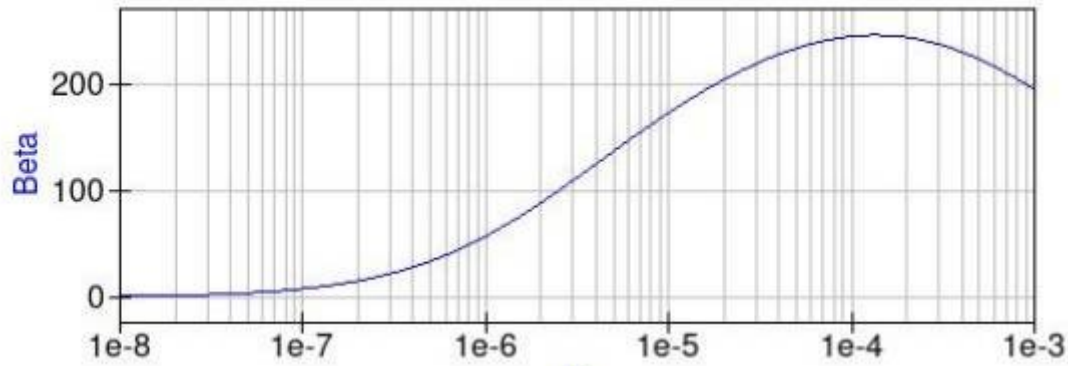

Equation
Eqn1
 $I_c = -V1 \cdot I$
 $\text{Beta} = I_c / I_b$

dc simulation

DC1

Parameter
sweep

SW1

Sim=DC1


Type=log

Param= I_b

Start=10n

Stop=1 m

811A Vacuum Tube Push-Pull Final

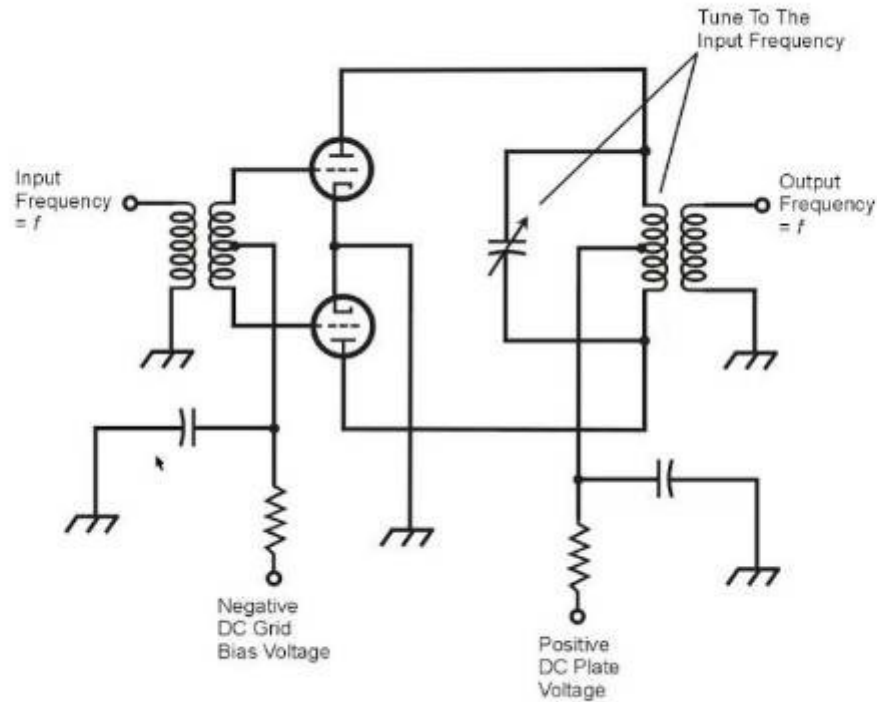


TOOLS


- Arduino UNO + Breadboard
- QUES – Quite Universal Circuit Simulator (Free)
 - <https://sourceforge.net/projects/qucs/files/latest/download>
- Circuit Calculations with Complex Numbers and Spreadsheets (Excel or LibreOffice CALC)
 - Free LibreOffice Download: <https://www.libreoffice.org/>
- Software Modems
- Software Defined Radios

Arduino and Breadboard

CQ CQ DE AE7OH K

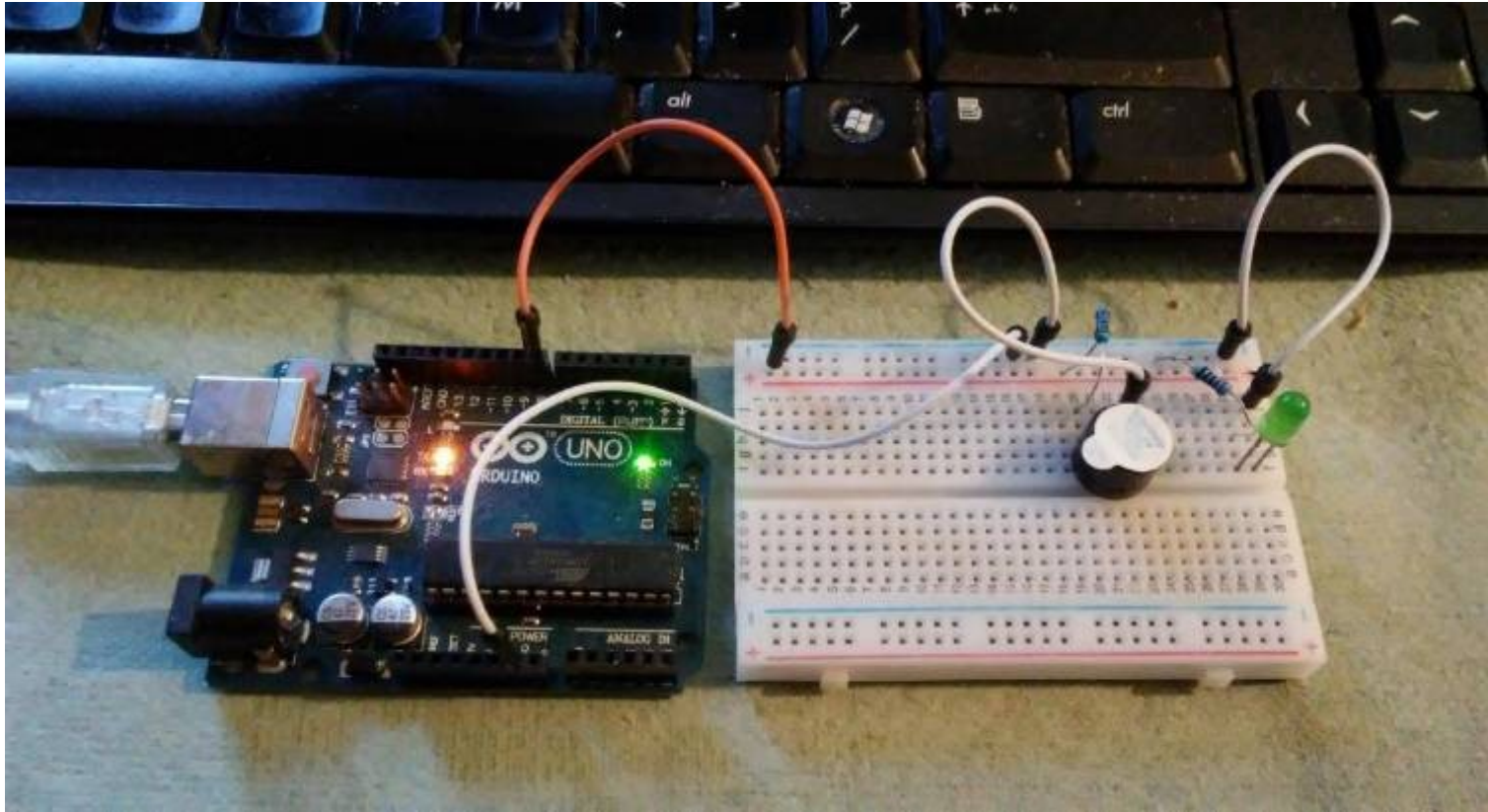


Arduino+Breadboard Schematic

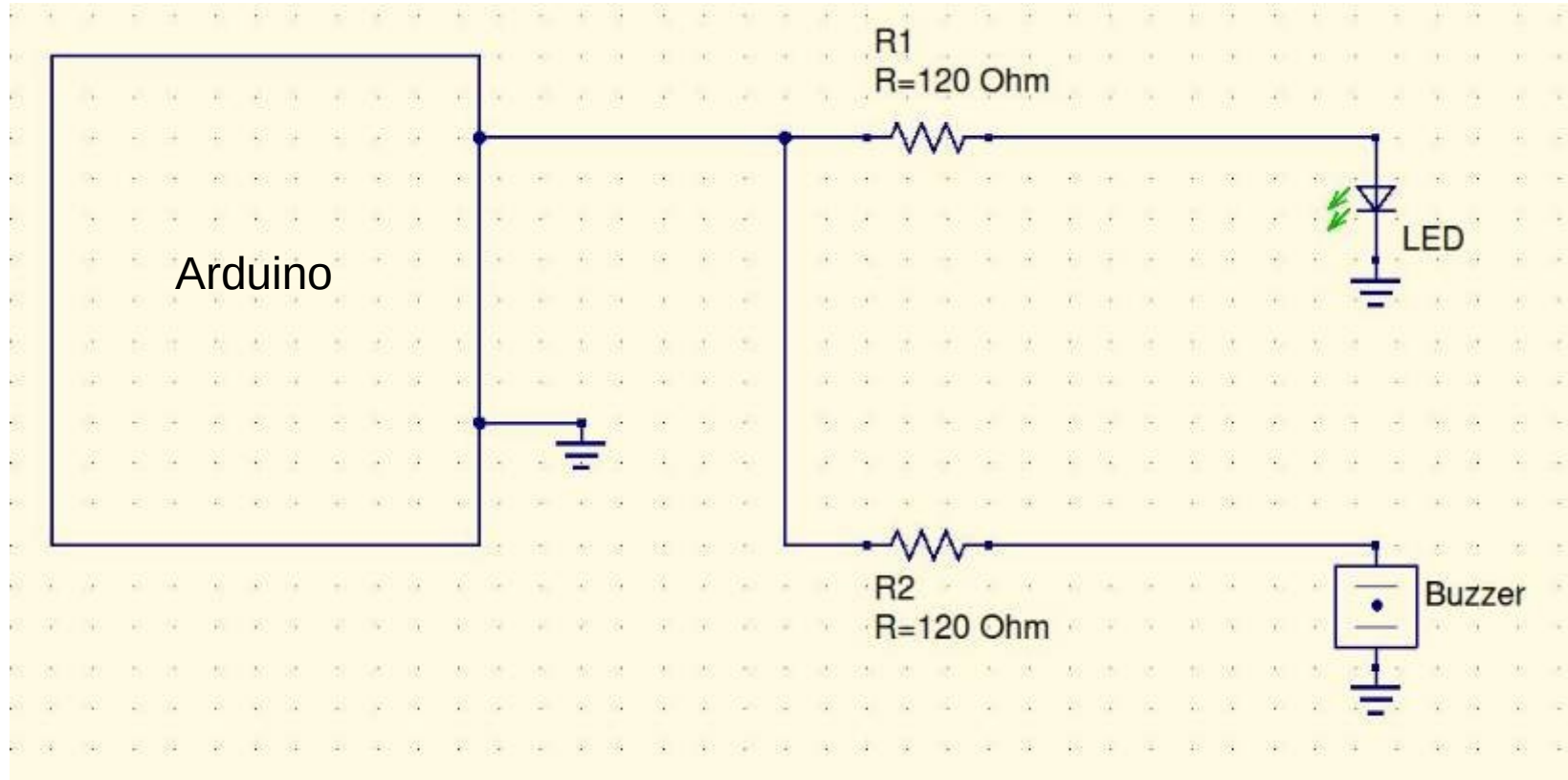

Quite Universal Circuit Simulator

<https://sourceforge.net/projects/qucs/files/latest/download>

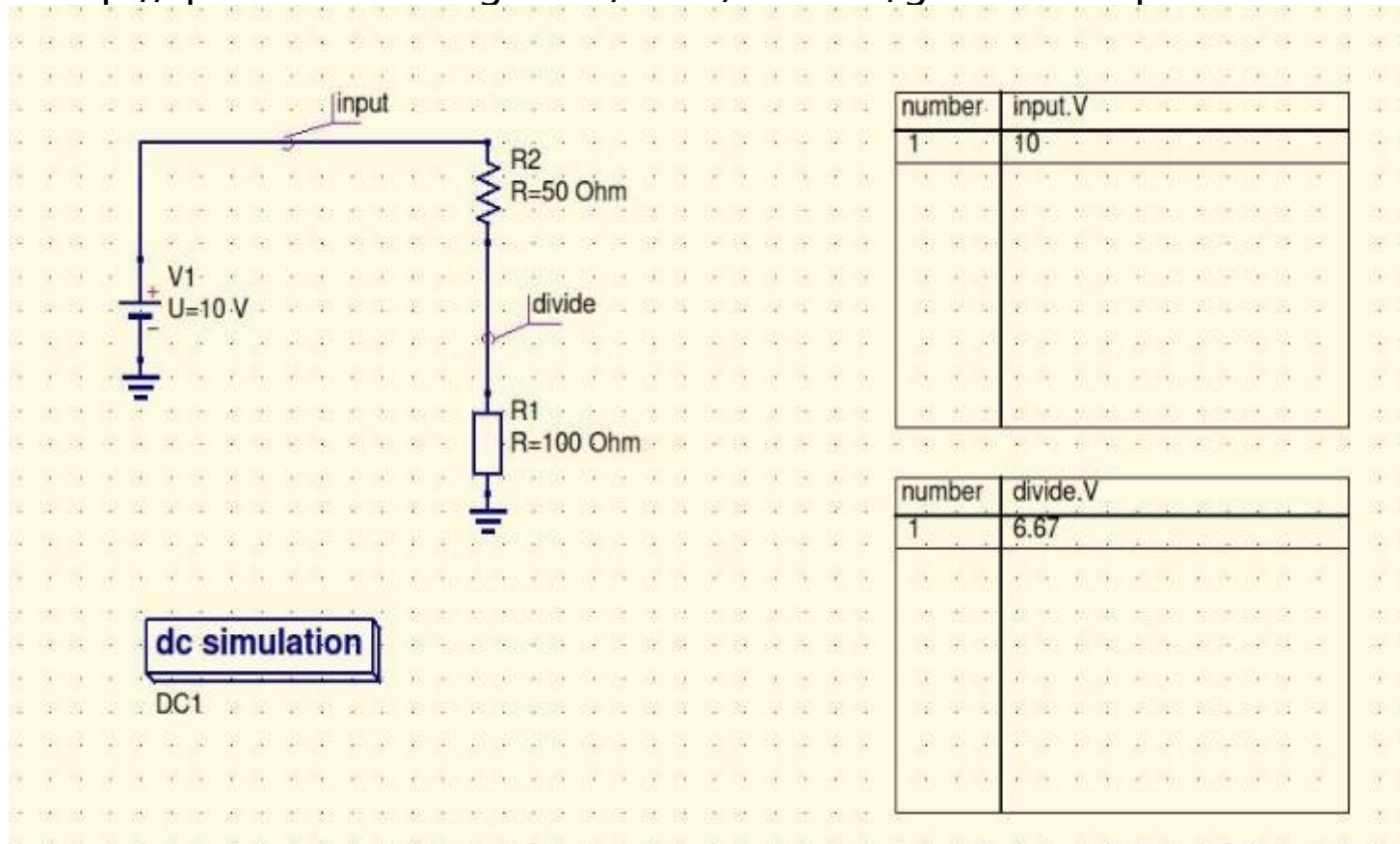
Manual: <http://qucs.sourceforge.net/docs/tutorial/getstarted.pdf>





RLC Transient Simulation

transient
simulation


TR1
Type=lin
Start=0
Stop=10 ms

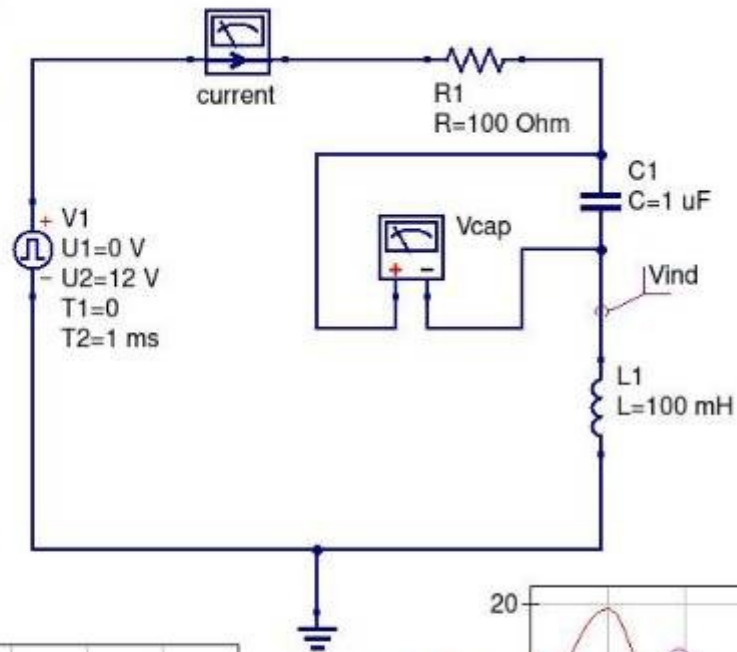

time	current.It	Vcap.Vt	Vind.Vt
0	0	0	0
0.000101	0.0113	0.587	10.3
0.000202	0.0205	2.21	7.74
0.000303	0.0268	4.63	4.69
0.000404	0.0299	7.52	1.49
0.000505	0.0299	10.6	-1.55
0.000606	0.0269	13.5	-4.15
0.000707	0.0217	15.9	-6.1
0.000808	0.0149	17.8	-7.27
0.000909	0.00729	18.9	-7.64
0.00101	-0.000903	19.3	-19.2
0.00111	-0.019	18.2	-16.3
0.00121	-0.0335	15.5	-12.2
0.00131	-0.0433	11.6	-7.29
0.00141	-0.0481	6.97	-2.16
0.00152	-0.0478	2.09	2.69
0.00162	-0.0429	-2.53	6.82

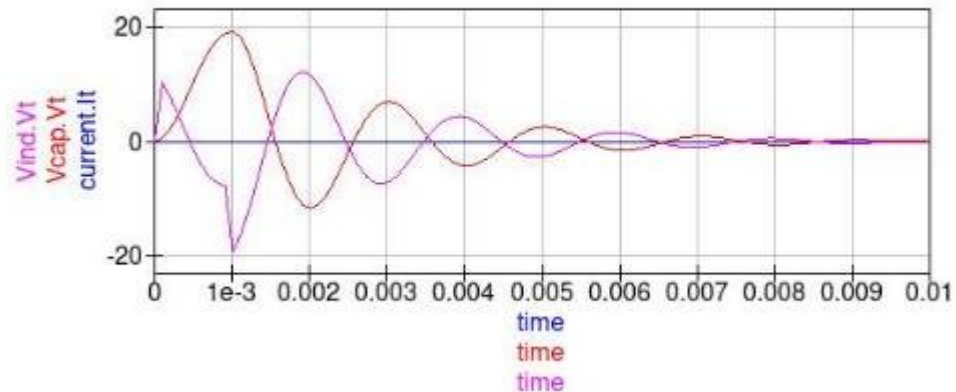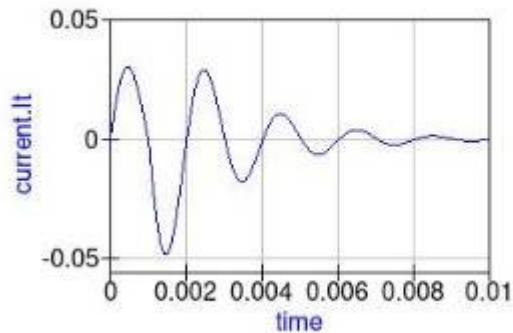

RLC Frequency And Transient Simulations


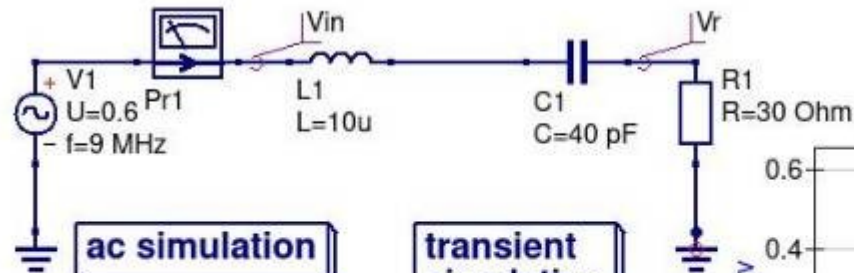


ac simulation


AC1
Type=lin
Start=4 MHz
Stop=12 MHz
Points=1001

transient simulation

TR1
Type=lin
Start=0
Stop=5 us

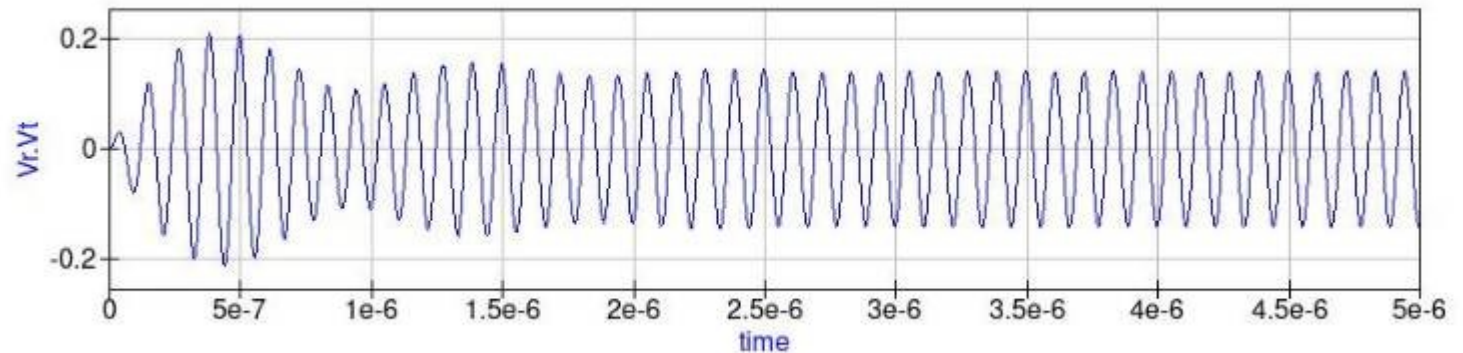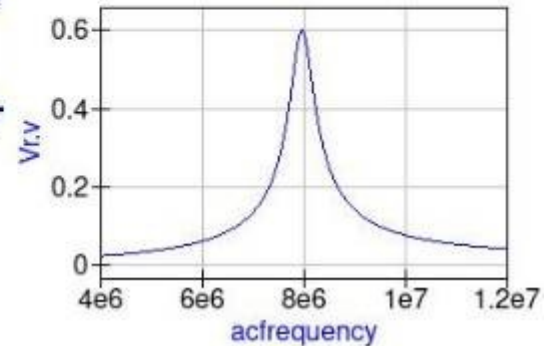





Simple Power Supply

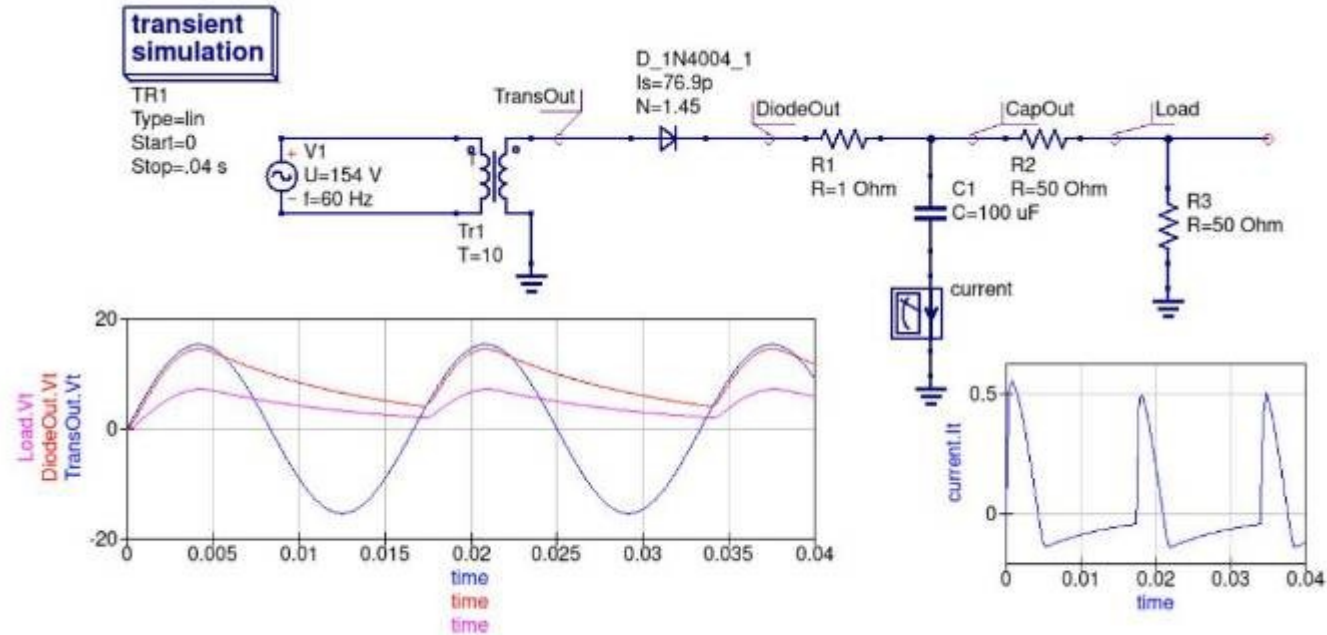



Regulated Power Supply

transient
simulation

TR1
Type=lin
Start=0
Stop=.05 s

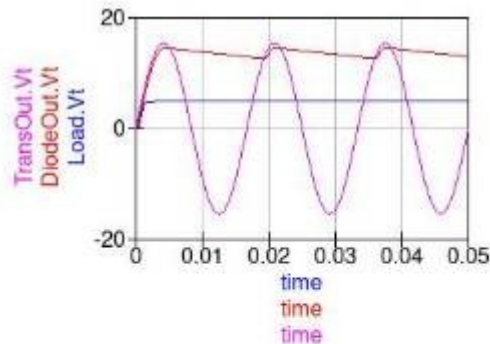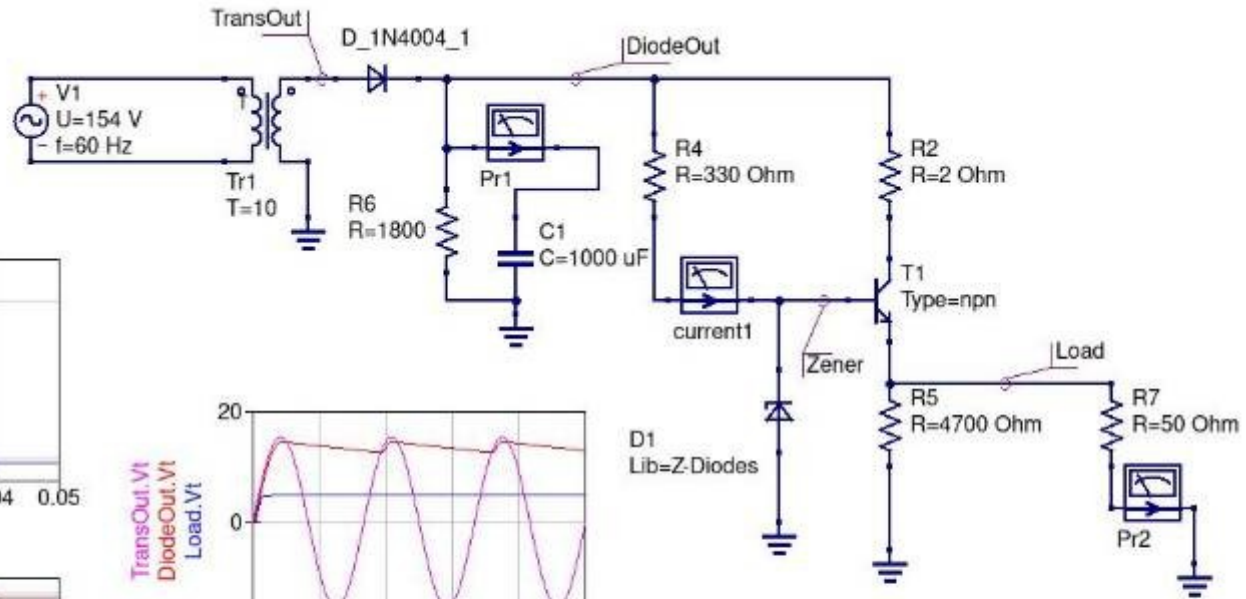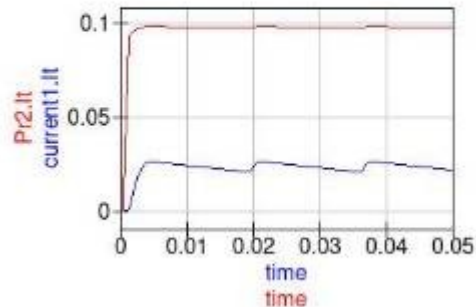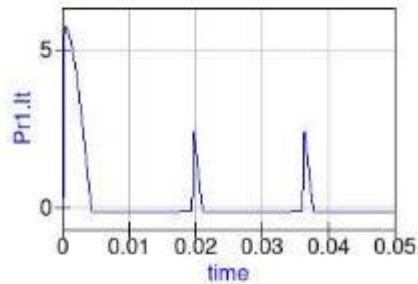

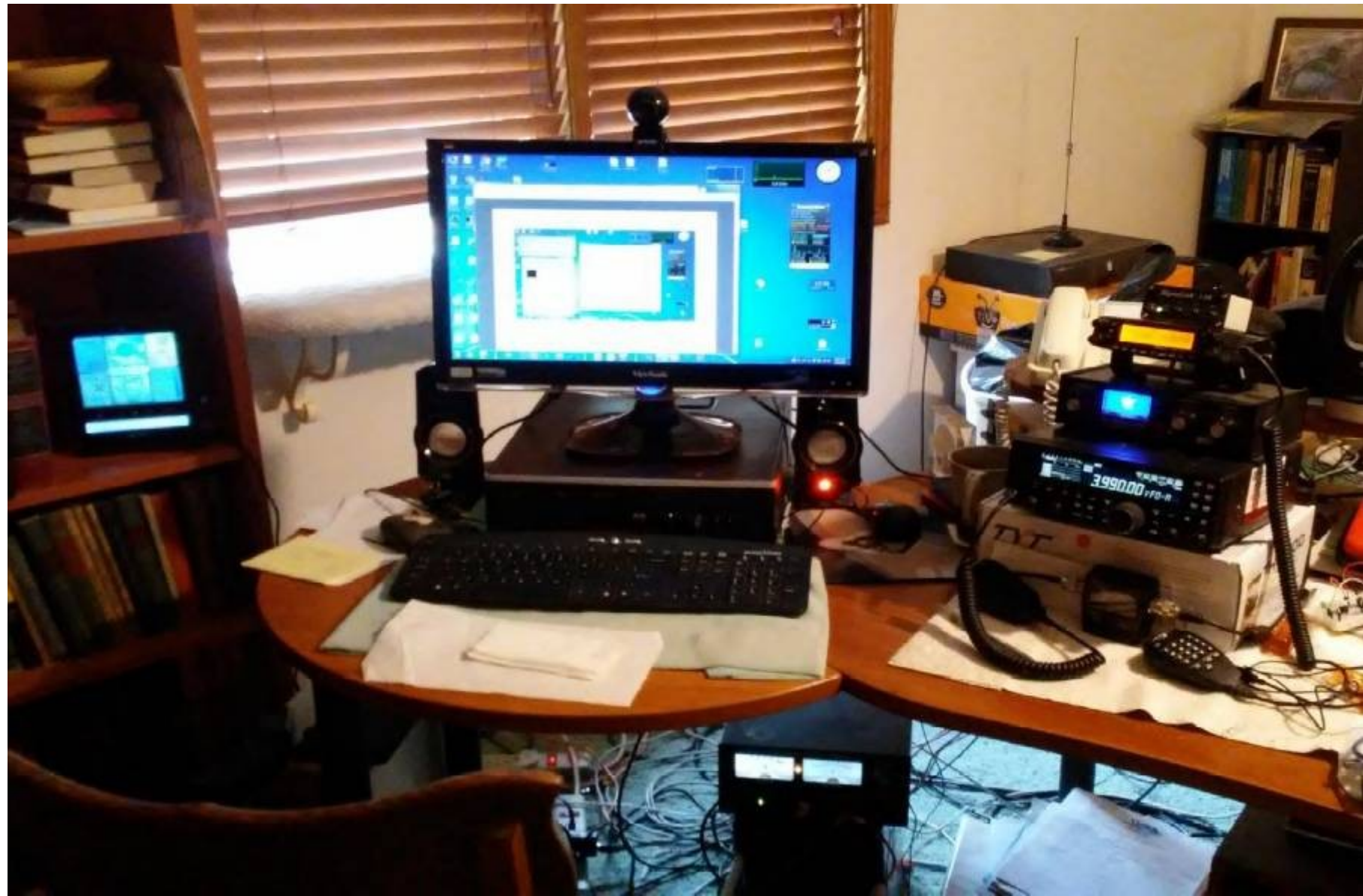

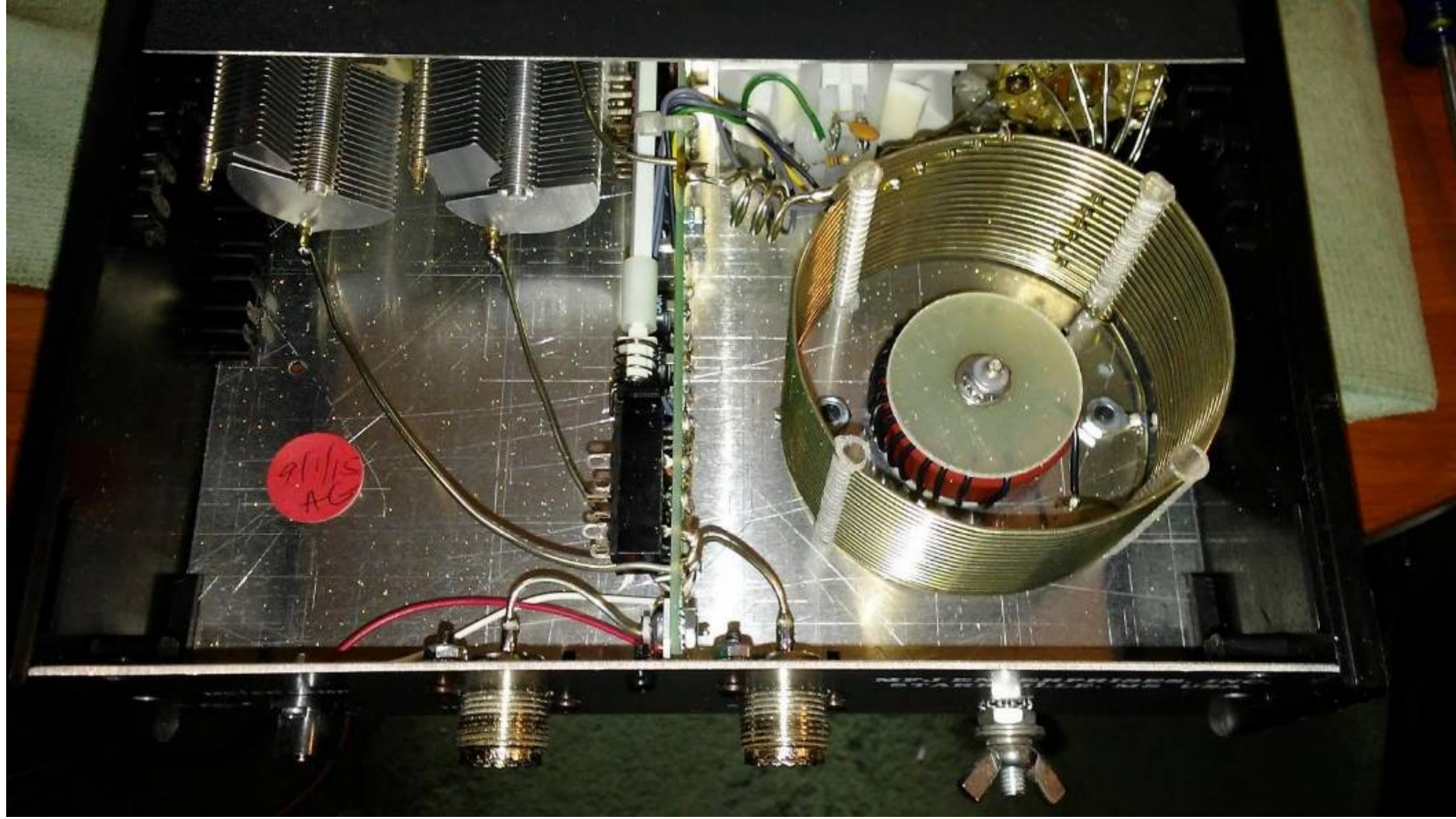


Alternating Current Sinusoids

imaginary




Radius rotates at f cycles per second to create sinusoid

real

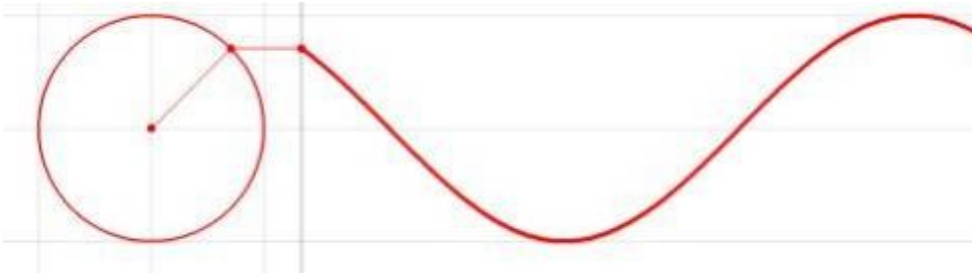


AC Representation Choice for Calculations

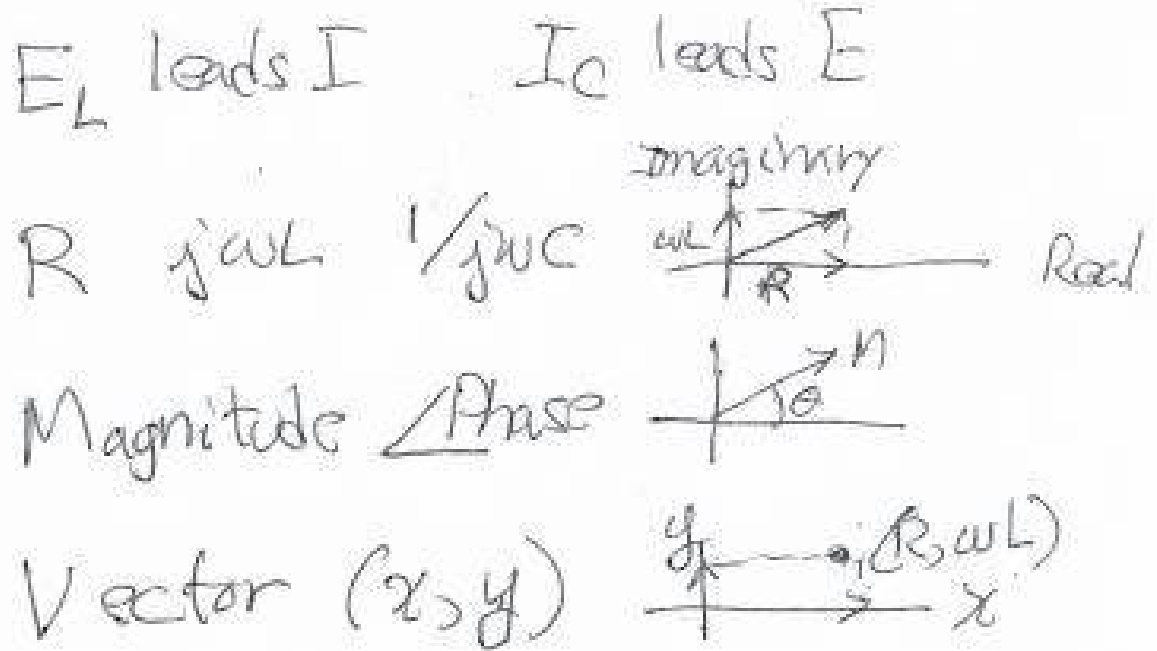- Eli the Ice man
- Complex Numbers
(easy calcs)
- Polar form
- Vectors



Calculate Tuned Antenna Impedance

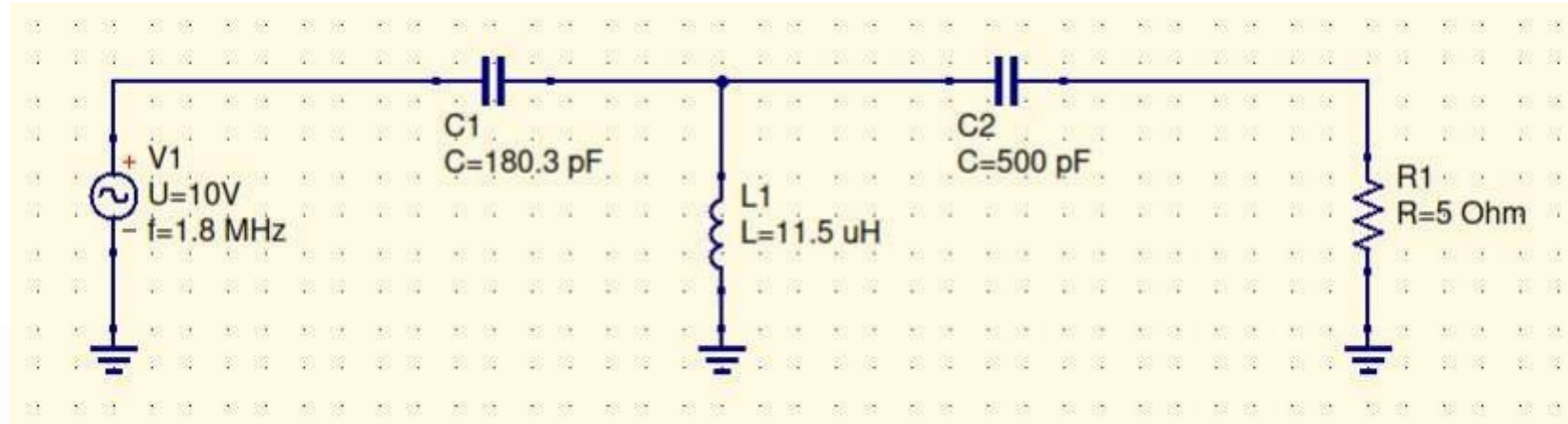

$$50 \Omega = \frac{1}{j\omega C_1} + \frac{1}{\frac{1}{j\omega L_1} + \frac{1}{R_1 + \frac{1}{j\omega C_2}}} \quad \begin{array}{l} \text{(IMPEDANCE)} \\ \text{(ADMITTANCE)} \\ \text{(IMPEDANCE)} \end{array}$$

Tuner Calc Spreadsheet

(See Figure 24.4 in Antenna Book)

	A	B	C	D	E	F	G	H
1				T NETWORK			ANTENNA	
2	component		C-xmtr		C-antenna		x	y
3				L				
4								
5								
6	value		1.80E-10 (180.3 pf)	1.15E-05 (11.5 uhenry)	5.00E-10 (500 pf)		5	0
7								
8								
9	reactance		-490.402038344852i	130.061826i	-176.838975027154i		5	
10								
11					38.2180330964639-2.79408640923299i			
12		freq	1.80E+06		answer			
13	radian freq	rad. Freq.	11309724					
14	(1.8 Mhz)							
15								
16		Q	1000	200	1000			
17			0.490402038344852-490.402038344852i	0.65030913+130.061826i	0.176838975027154-176.838975027154i		5	
18								
19				per Figure 24.4 Antenna Book	49.0615676552388-4.68763200560596i			
20					answer			


=IMSUM(C9,IMDIV(1,IMSUM(IMDIV(1,D9),IMDIV(1,IMSUM(E9,G9))))))

Excel or CALC Complex Functions

COMPLEX	Returns a complex number, given real and imaginary parts as numbers.	IMLOG10	Returns the base-10 logarithm of a complex number.
IMABS	Returns the absolute value of a complex number.	IMLOG2	Returns the base-2 logarithm of a complex number.
IMAGINARY	Returns the imaginary part of a complex number.	IMPOWER	Returns a complex number raised to a power.
IMARGUMENT	Returns the argument of a complex number.	IMPRODUCT	Returns the product of complex numbers.
IMCONJUGATE	Returns the complex conjugate of a complex number.	IMREAL	Returns the real part of a complex number.
IMCOS	Returns the cosine of a complex number.	IMSEC	Returns the secant of a complex number.
IMCOSH	Returns the hyperbolic cosine of a complex number.	IMSECH	Returns the hyperbolic secant of a complex number.
IMCSC	Returns the cosecant of a complex number.	IMSIN	Returns the sine of a complex number.
IMCSCH	Returns the hyperbolic cosecant of a complex number.	IMSINH	Returns the hyperbolic sine of a complex number.
IMCOT	Returns the cotangent of a complex number.	IMSQRT	Returns the square root of a complex number.
IMDIV	Returns the result of dividing one complex number by another.	IMSUB	Returns the difference between 2 complex numbers.
IMEXP	Returns e to the power of a complex number.	IMSUM	Returns the sum of complex numbers.
IMLN	Returns the natural logarithm of a complex number.	IMTAN	Returns the tangent of a complex number.

Tuner Adjustments


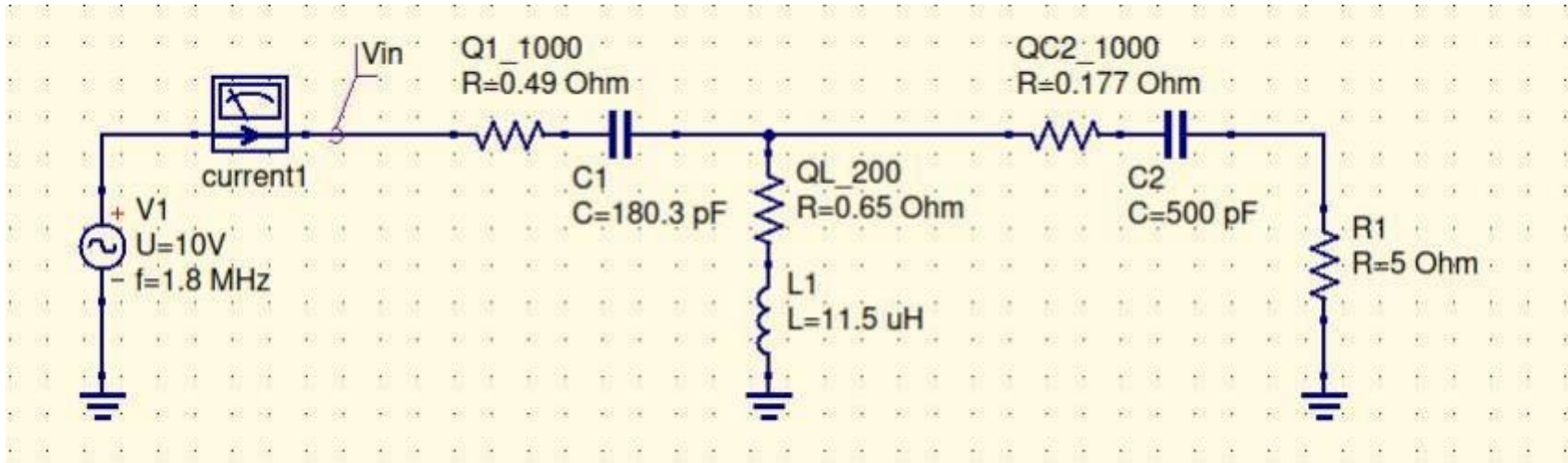
- Tuner adjusted 5-Ohm Antenna to 38 ohms
- Ant. Book assumed Q-values for components
- Added Q-Resistors yield 50 ohms



Tuner Reactance Tweaks

- Minor phase error in answer can be removed by changing C1 to zero the reactance error
- C2 can be adjusted to compensate for a reactive component in the Antenna:
 - Decrease C2 to compensate for inductive antenna
 - Increase C2 to compensate for capacitive antenna
- Antenna design would probably try to make antenna nearer to the ideal 50-ohm, 0-reactance impedance at the desired frequency(s)
- Stay tuned!

Match1

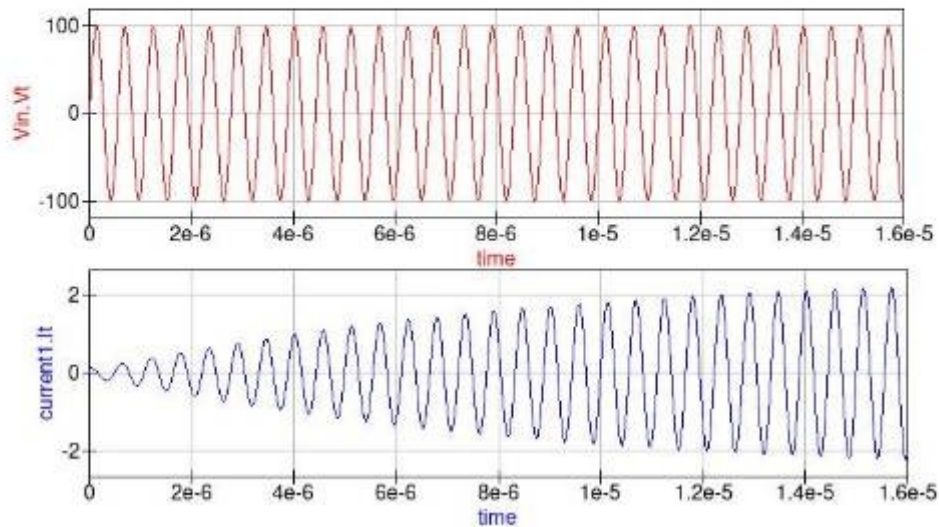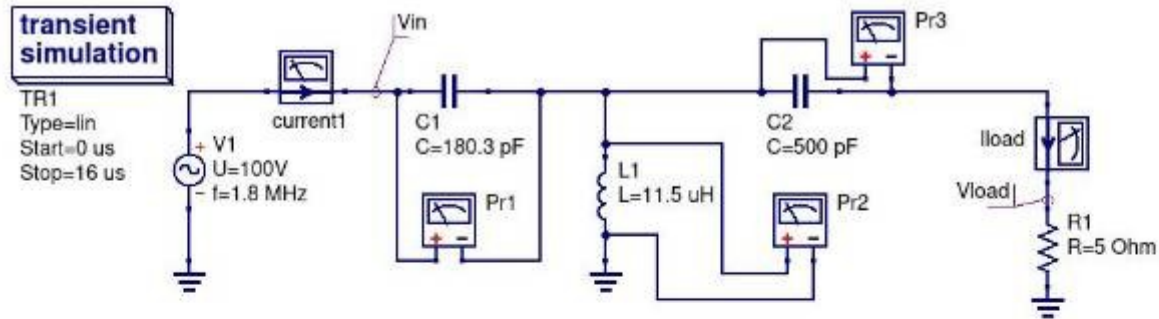



ac simulation

AC1
Type=lin
Start=1.5 MHz
Stop=2 MHz

Match2

Input voltage: 100V

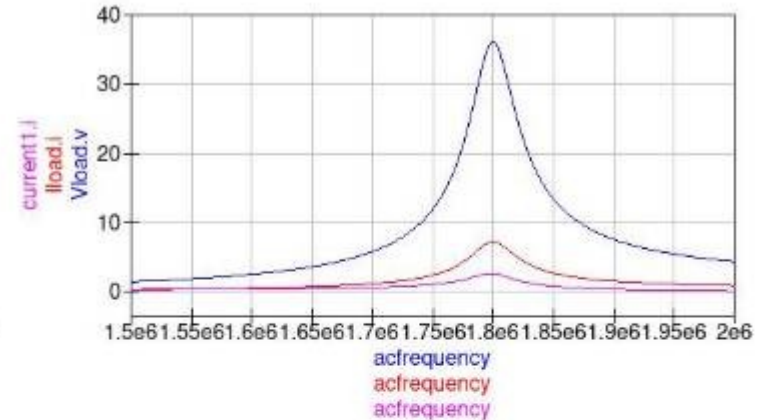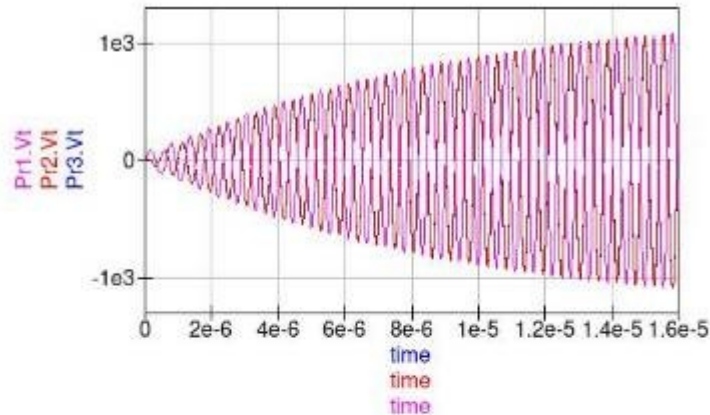But peak voltages
across tuner
elements are 1000V



time	Vin.Vt	Pr1.Vt	Pr2.Vt	Pr3.Vt	Vload.Vt
1.57e-5	98.7	-100	199	229	-29.6
1.57e-5	100	94.2	5.79	36.1	-30.3
1.57e-5	98	286	-188	-158	-30.1
1.57e-5	92.9	468	-375	-346	-28.8
1.57e-5	84.7	635	-550	-524	-26.6
1.58e-5	73.8	782	-708	-684	-23.5
1.58e-5	60.4	903	-842	-823	-19.6
1.58e-5	45.1	994	-949	-934	-15.1
1.58e-5	28.3	1.05e+03	-1.03e+03	-1.02e+03	-10.2
1.58e-5	10.5	1.08e+03	-1.07e+03	-1.06e+03	-4.83
1.58e-5	-7.53	1.07e+03	-1.08e+03	-1.08e+03	0.659
1.59e-5	-25.4	1.02e+03	-1.05e+03	-1.06e+03	6.13
1.59e-5	-42.4	945	-987	-999	11.4


acfrequency	Iload.i	Vload.v
1.8e6	-7.07-j0.897	-35.4-j4.49
1.8e6	-7.12-j0.713	-35.6-j3.57
1.8e6	-7.16-j0.525	-35.8-j2.63
1.8e6	-7.19-j0.335	-35.9-j1.68
1.8e6	-7.21-j0.143	-36-j0.717
1.8e6	-7.21+j0.0494	-36.1+j0.247
1.8e6	-7.21+j0.242	-36.1+j1.21
1.8e6	-7.2+j0.434	-36+j2.17
1.8e6	-7.18+j0.625	-35.9+j3.13
1.8e6	-7.14+j0.813	-35.7+j4.07
1.8e6	-7.1+j0.999	-35.5+j4.99
1.8e6	-7.05+j1.18	-35.2+j5.9
1.8e6	-6.99+j1.36	-34.9+j6.79

High RF Tuner Voltages

- High Voltage in tuner elements
 - 100 volts peak source
 - 1000 volts peak across components
- Arcing and RF burns potential
- Solutions include better antenna design
 - e.g., a Balun can help match



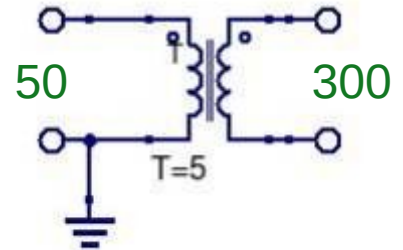Example: 5:1 transformer
Matches 50 ohm coax
To 300 ohm antenna




Internet Antenna



CHA TD LITE HF Antenna



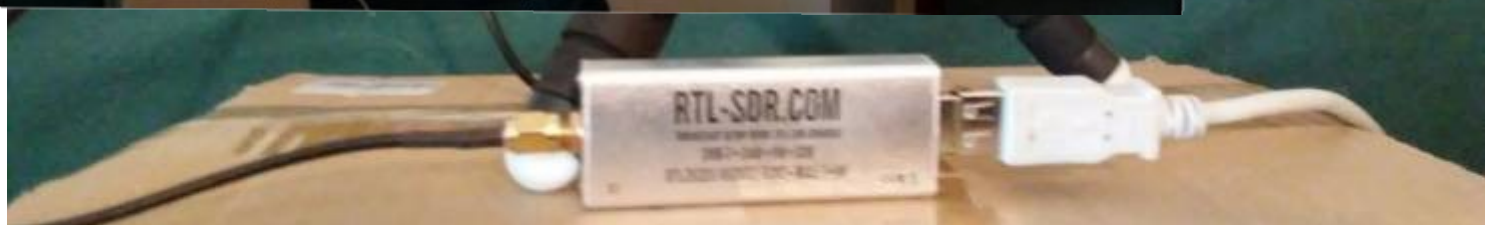


RTL-SDR Software Defined Radio




FM Radio Station

GQRX
(Linux)
or
SDR-Sharp

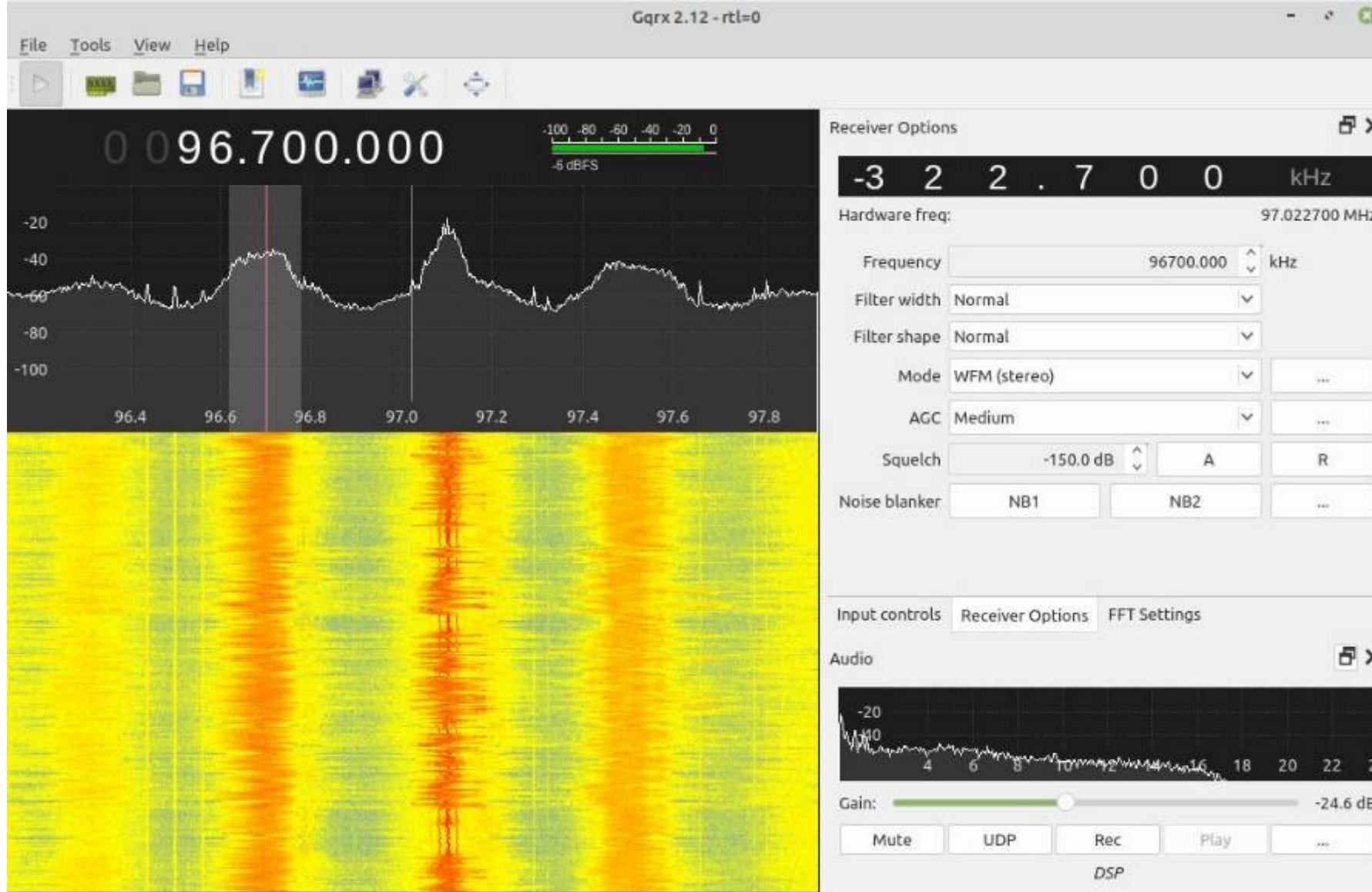

SDR

VHF
Station

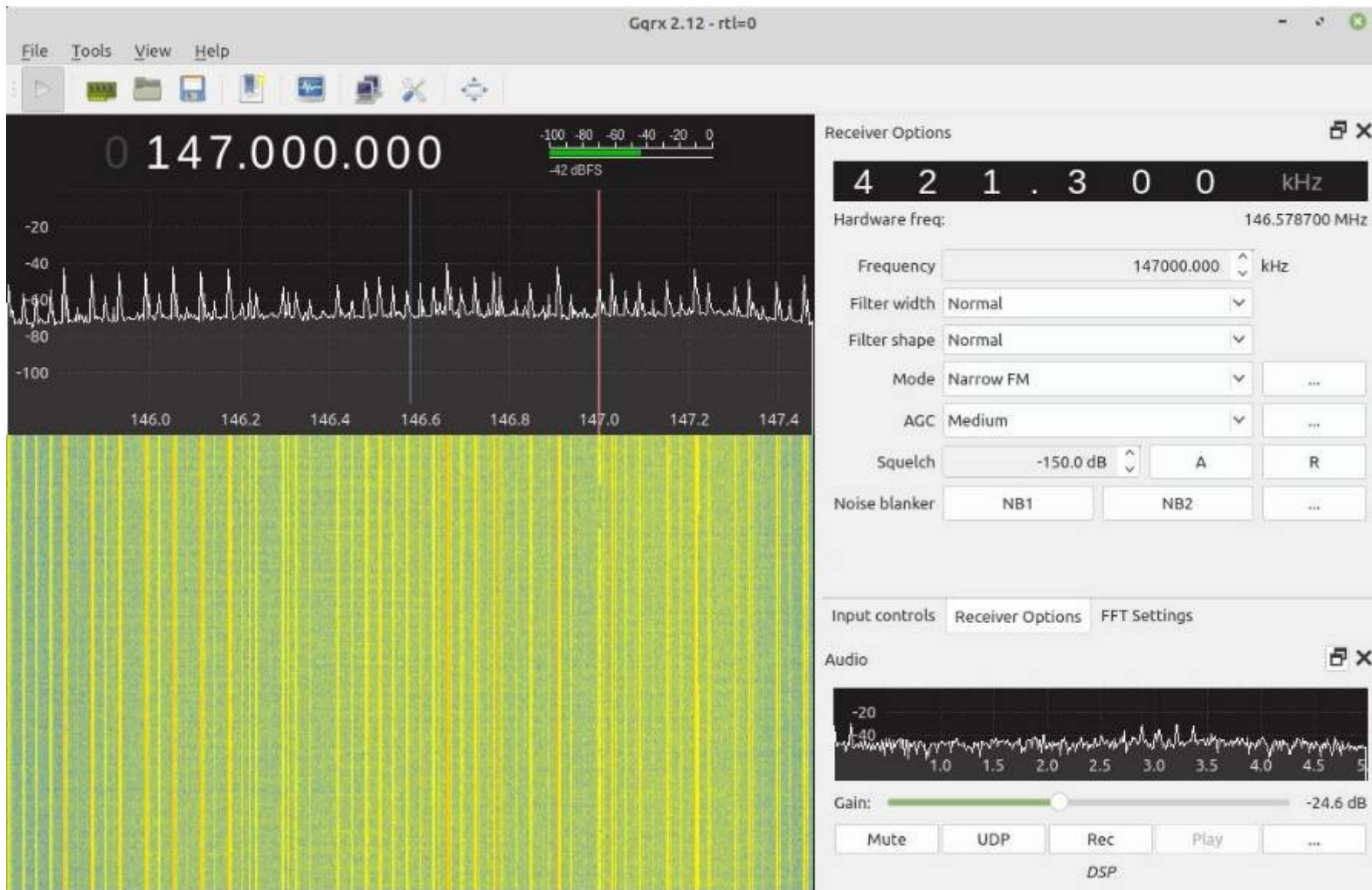

Handhelds



20 Meter Antenna

